

# Electric Energy and Circuits

## Solutions for Practice Problems

Student Textbook page 610

### 1. Frame the Problem

- By definition the potential difference between anode and cathode is the quotient of the change in the electric potential energy of charges passing between electrodes and the quantity of the charge.
- The electric potential energy is equal to the amount of work done.
- The expression that defines potential difference applies to this problem.

### Identify the Goal

The potential difference of the battery,  $V$

### Variables and Constants

Involved in the Problem	Known	Unknown
$W$	$W = 7.50 \times 10^{-2} \text{ J}$	$V$
$\Delta E_Q$	$Q = 3.75 \times 10^{-3} \text{ J}$	$\Delta E_Q$
$V$		
$Q$		

### Strategy

Use the expression for potential difference.

The amount of work done is equal to the potential energy.

Substitute in the variables.

Divide

Since  $1 \frac{\text{J}}{\text{C}}$  is equivalent to 1 V, thus

The potential difference is 20.0 V.

### Calculations

$$V = \frac{\Delta E_Q}{Q}$$

$$W = \Delta E_Q$$

$$W = 7.50 \times 10^{-2} \text{ J}$$

$$\Delta E_Q = 3.75 \times 10^{-3} \text{ C}$$

$$V = \frac{7.5 \times 10^{-2} \text{ J}}{3.75 \times 10^{-3}}$$

$$V = 20.0 \text{ V}$$

### Validate

The unit for potential difference is the volt.

### 2. Frame the Problem

- The work done transforms chemical potential energy into electric potential energy. Thus, the electric potential energy is equal to the amount of work done.
- The expression that defines potential difference applies to this problem.

### Identify the Goal

The amount of work that has been done on the charge

**Variables and Constants****Involved in the Problem** $W$  $\Delta E_Q$  $V$  $Q$ **Known** $V = 9 \text{ V}$  $Q = 4.20 \times 10^{-2} \text{ C}$ **Unknown** $W$  $\Delta E_Q$ **Strategy**

Use the expression for the potential difference.

Solve for  $\Delta E_Q$ .

Since 1 V·C is equal to 1 J, then

Since 1 V·C is equal to 1 J, then

The amount of work done is equal to the potential energy.

Since 1 V·C is equivalent to 1 J, thus

The amount of work done on the charge is 0.378 J.

**Calculations**

$$V = \frac{\Delta E_Q}{Q}$$

Substitute first

$$9\text{V} = \frac{\Delta E_Q}{4.20 \times 10^{-2} \text{ C}}$$

$$(9\text{V})(4.20 \times 10^{-2} \text{ C}) = \frac{\Delta E_Q}{4.20 \times 10^{-2} \text{ C}}$$

$$\Delta E_Q = 0.378 \text{ J}$$

Solve for  $\Delta E_Q$  first

$$VQ = \frac{\Delta E_Q}{Q} Q$$

$$\Delta E_Q = (9 \text{ V})(4.20 \times 10^{-2} \text{ C})$$

$$\Delta E_Q = 0.378 \text{ J}$$

$$W = \Delta E_Q$$

$$W = 0.378 \text{ J}$$

**Validate**

The units combined to give joules, which is the correct unit for work.

**3. Frame the Problem**

- The electric potential energy is equal to the amount of work done.
- The expression that defines potential difference applies to this problem.

**Identify the Goal**

The amount of charge that was moved

**Variables and Constants****Involved in the Problem** $W$  $\Delta E_Q$  $V$  $Q$ **Known** $W = 0.75 \text{ J}$  $V = 12 \text{ V}$ **Unknown** $Q$  $\Delta E_Q$ **Strategy**

Use the expression for the potential difference.

The amount of work done is equal to the potential energy.

**Calculations**

$$V = \frac{\Delta E_Q}{Q}$$

$$W = \Delta E_Q$$

$$W = 0.75 \text{ J}$$

Solve for the charge.

$$\begin{aligned} \text{Substitute first} \\ (12\text{V})Q &= \frac{0.75\text{J}}{Q} Q \\ \frac{(+12\text{V})Q}{+12\text{V}} &= \frac{0.75\text{J}}{12\text{V}} \\ Q &= \frac{0.75\text{J}}{12\text{V}} \end{aligned}$$

Since  $1 \frac{\text{J}}{\text{V}}$  is equivalent to 1 C, thus

The charge is  $6.3 \times 10^{-2}$  C.

Solve for  $Q$  first

$$\begin{aligned} VQ &= \frac{\Delta E_Q}{Q} Q \\ \frac{+Q}{+} &= \frac{\Delta E_Q}{V} \\ Q &= \frac{0.75\text{J}}{12\text{V}} \end{aligned}$$

$$Q = 6.3 \times 10^{-2} \text{ C}$$

**Validate**

The answer is in coulombs, which is the correct unit for charge.

**Solutions for Practice Problems**

Student Textbook page 614

**4. Frame the Problem**

- The potential difference drives a current through the circuit.
- The amount of work done by the current is the same as the change in the potential energy of the charges as they move through the circuit.
- The expressions that define potential difference and current apply to this problem.

**Identify the Goal**

To find the potential difference of the battery

**Variables and Constants**

**Involved in the Problem**

$I$   
 $\Delta E_Q$   
 $W$   
 $V$   
 $\Delta t$   
 $Q$

**Known**

$I = 2.25 \text{ A}$   
 $W = 8.10 \times 10^2 \text{ J}$   
 $\Delta t = 1.5 \text{ min}$

**Unknown**

$V$   
 $\Delta E_Q$   
 $Q$

**Strategy**

Convert time to SI units.

Use the definition for current to find the amount of charge.

**Calculations**

$$1.5 \text{ min} \frac{60 \text{ s}}{\text{min}} = 90 \text{ s}$$

$$I = \frac{Q}{\Delta t}$$

Substitute first

$$(2.25 \text{ A})(90 \text{ s}) = \frac{Q}{90\text{s}} (90\text{s})$$

$$Q = (2.25 \text{ A})(90 \text{ s})$$

$$Q = 202.5 \text{ C}$$

Solve for  $Q$  first

$$I\Delta t = \frac{Q}{\Delta t} \Delta t$$

$$Q = (2.25 \text{ A})(90 \text{ s})$$

Since 1 A·s is equivalent to 1 C, thus

The amount of work done is equal to the potential energy.

Use the expression for potential difference.

Substitute in the values.

$$W = \Delta E_Q$$

$$W = 8.10 \times 10^2 \text{ J}$$

$$\Delta E_Q = 8.10 \times 10^2 \text{ J}$$

$$V = \frac{\Delta E_Q}{Q}$$

$$V = \frac{8.10 \times 10^2 \text{ J}}{202.5 \text{ C}}$$

Divide  $4.0 \frac{\text{J}}{\text{C}}$   
 Since  $1 \frac{\text{J}}{\text{C}}$  is equivalent to 1 V, thus  $V = 4.0 \text{ V}$

The potential difference is 4.0 V.

### Validate

The units combined to give volts, which is the correct unit for potential difference.

## 5. Frame the Problem

- The battery is sending a current that does a known amount of work by moving an amount of charge through the circuit.
- The amount of work done by the current is the same as the change in the potential energy of the charges as they move through the circuit.

### Identify the Goal

The time required to do a given amount of work

### Variables and Constants

#### Involvement in the Problem

$I$

$\Delta E_Q$

$W$

$V$

$\Delta t$

$Q$

#### Known

$I = 5.0 \text{ A}$

$W = 680 \text{ J}$

$V = 17 \text{ V}$

#### Unknown

$\Delta t$

$\Delta E_Q$

$Q$

### Strategy

The amount of work done is equal to the potential energy.

Use the expression for potential difference.

### Calculations

$$W = \Delta E_Q$$

$$W = 680 \text{ J}$$

$$\Delta E_Q = 680 \text{ J}$$

$$V = \frac{\Delta E_Q}{Q}$$

Substitute first

$$(17 \text{ V})Q = \frac{680 \text{ J}}{Q} \text{ C}$$

$$\frac{(17 \text{ V})Q}{17 \text{ V}} = \frac{680 \text{ J}}{17 \text{ V}}$$

$$Q = \frac{680 \text{ J}}{17 \text{ V}}$$

$$Q = 40 \text{ C}$$

$$I = \frac{Q}{\Delta t}$$

Substitute first

$$(5.0 \text{ A})\Delta t = \frac{40 \text{ C}}{\Delta t} \Delta t$$

$$\Delta t = \frac{40 \text{ C}}{5.0 \text{ A}}$$

Since  $1 \frac{\text{J}}{\text{V}}$  is equivalent to 1 C, therefore

Use the definition for current to solve for the amount of time.

Since 1 C is equal to 1 A·s,  $\Delta t = 8 \text{ s}$

$1 \frac{\text{C}}{\text{A}}$  is equivalent to 1 s.

It would take 8 s for the battery to do the amount of work.

Solve for  $Q$  first

$$VQ = \frac{\Delta E_Q}{Q} \text{ C}$$

$$\frac{VQ}{V} = \frac{\Delta E_Q}{V}$$

$$Q = \frac{680 \text{ J}}{17 \text{ V}}$$

Solve for  $\Delta t$  first

$$I\Delta t = \frac{Q}{\Delta t} \Delta t$$

$$I\frac{\Delta t}{I} = \frac{Q}{I}$$

$$\Delta t = \frac{40 \text{ C}}{5.0 \text{ A}}$$

**Validate**

The work and the potential difference were used to find the charge. Then the amount of charge and the value of the current were used to find the time that was needed to do the work. The answer is in seconds, which is the correct unit for time.

**6. Frame the Problem**

- The battery is sending a current that does an unknown amount of work by moving an amount of charge through the circuit.
- The amount of work done by the current is the same as the change in the potential energy of the charges as they move through the circuit.

**Identify the Goal**

To find the amount of work done by the battery

**Variables and Constants****Involved in the Problem** $I$  $\Delta E_Q$  $W$  $V$  $\Delta t$  $Q$ **Known** $I = 4.70 \text{ A}$  $V = 25.0 \text{ V}$  $\Delta t = 36.0 \text{ s}$ **Unknown** $Q$  $\Delta E_Q$  $W$ **Strategy**

Use the definition for current to find the amount of charge.

Since 1 A·s is equivalent to 1 C, therefore

Use the expression for potential difference.

Since 1 V·C is equivalent to 1 J, thus

The amount of work done is equal to the potential energy.

The amount of work done is  $4.23 \times 10^3 \text{ J}$ .

**Calculations**

$$I = \frac{Q}{\Delta t}$$

Substitute first

$$(4.70 \text{ A})(36.0 \text{ s}) \\ = \frac{Q}{36.0 \text{ s}}(36.0 \text{ s})$$

$$Q = (4.70 \text{ A})(36.0 \text{ s})$$

$$Q = 169.2 \text{ C}$$

$$V = \frac{\Delta E_Q}{Q}$$

Substitute first

$$25.0 \text{ V} = \frac{\Delta E_Q}{169.2 \text{ C}} \\ (25.0 \text{ V})(169.2 \text{ C}) \\ = \frac{\Delta E_Q}{169.2 \text{ C}}(169.2 \text{ C})$$

$$\Delta E_Q = 4.23 \times 10^3 \text{ J}$$

$$W = \Delta E_Q$$

$$W = 4.23 \times 10^3 \text{ J}$$

Solve for  $Q$  first

$$I\Delta t = \frac{Q}{\Delta t}\Delta t$$

$$Q = (4.70 \text{ A})(36.0 \text{ s})$$

Solve for  $\Delta E_Q$  first

$$VQ = \frac{\Delta E_Q}{Q}Q$$

$$\Delta E_Q = (25.0 \text{ V})(169.2 \text{ J})$$

$$\Delta E_Q = 4.23 \times 10^3 \text{ J}$$

**Validate**

The current and the time were used to find the charge. Then the amount of charge and the value of the potential difference were used to find the work.

The units combined to give joules, which is the correct unit for work.

**7. Frame the Problem**

- The battery is sending a current that does a known amount of work by moving an amount of charge through the circuit.
- Potential energy, potential difference, and charge are all related.
- Charge, current, and time are all related.

**Identify the Goal**

To find the current through the battery

**Variables and Constants**

Involved in the Problem	Known	Unknown
$I$	$W = 9.6 \times 10^5 \text{ J}$	$Q$
$Q$	$V = 160 \text{ V}$	$I$
$V$	$\Delta t = 2 \text{ min}$	
$\Delta t$		
$W$		

**Strategy**

Convert time to SI units.

Use the expression for potential difference to solve for the charge. Remember that  $W$  is equal to  $\Delta E_Q$ .

**Calculations**

$$2 \text{ min} \frac{60 \text{ s}}{1 \text{ min}} = 180 \text{ s}$$

$$V = \frac{W}{Q}$$

Substitute first

$$(160 \text{ V})Q = \frac{9.6 \times 10^5 \text{ J}}{Q}$$

$$\frac{(160 \text{ V})Q}{160 \text{ V}} = \frac{9.6 \times 10^5 \text{ J}}{160 \text{ V}}$$

$$Q = \frac{9.6 \times 10^5 \text{ J}}{160 \text{ V}}$$

$$Q = 6000 \text{ C}$$

$$I = \frac{Q}{\Delta t}$$

$$I = \frac{6000 \text{ C}}{180 \text{ s}}$$

$$I = 50 \text{ A}$$

Solve for  $Q$  first

$$VQ = \frac{\Delta E_Q}{Q}$$

$$\frac{VQ}{V} = \frac{\Delta E_Q}{V}$$

$$Q = \frac{9.6 \times 10^5 \text{ J}}{160 \text{ V}}$$

Since  $1 \frac{\text{J}}{\text{V}}$  is equivalent to 1 C, therefore

Use the definition of current.

Divide

Since  $1 \frac{\text{C}}{\text{s}}$  is equivalent to 1 A,

The current is 50 A.

**Validate**

The answer is in amperes, which is the correct unit for current.

**8. Frame the Problem**

- The light draws a current through it.
- Charge, current, and time are all related.

**Identify the Goal**

To find the time it will take for the light to draw a charge of 36 C.

**Variables and Constants****Involved in the Problem** $I$  $Q$  $\Delta t$ **Known**

$I = 0.48 \text{ A}$

$Q = 36 \text{ C}$

**Unknown** $\Delta t$ **Strategy**

Use the definition for current to find the amount of time.

**Calculations**

$$I = \frac{Q}{\Delta t}$$

Substitute first

$$(0.48 \text{ A})\Delta t = \frac{36 \text{ C}}{\Delta t} \Delta t$$

$$\Delta t = \frac{36 \text{ C}}{0.48 \text{ A}}$$

$$\Delta t = 75 \text{ s}$$

Solve for  $\Delta t$  first

$$I\Delta t = \frac{Q}{\Delta t} \Delta t$$

$$\frac{\Delta t}{\cancel{\Delta t}} I = \frac{Q}{I}$$

$$\Delta t = \frac{36 \text{ C}}{0.48 \text{ A}}$$

$$\Delta t = 75 \text{ s}$$

Since  $1 \frac{\text{C}}{\text{A}}$  is equivalent to 1 s,

The time it takes for 36 C of charge to pass through the wire is 75 s.

**Validate**

The answer is in seconds, which is the correct unit for time.

**9. Frame the Problem**

- The electric circuit draws a current through it.
- Charge, current, and time are all related.

**Identify the Goal**

To find the time it will take for the light to draw a charge of 36 C.

**Variables and Constants****Involved in the Problem** $I$  $Q$  $\Delta t$  $V$ **Known**

$\Delta t = 1 \text{ h}$

$I = 20 \text{ A}$

$V = 120 \text{ V}$

**Unknown** $Q$ **Strategy**

Convert time to SI units.

Use the definition for current to solve for the charge. Remember that A·s is equivalent to 1 C.

**Calculations**

$$1 \text{ h} \left( \frac{60 \text{ min}}{\text{h}} \right) \left( \frac{60 \text{ s}}{\text{min}} \right) = 3600 \text{ s}$$

$$I = \frac{Q}{\Delta t}$$

Substitute first

$$\begin{aligned} (20 \text{ A})(3600 \text{ s}) \\ = \frac{Q}{3600 \text{ s}}(3600 \text{ s}) \end{aligned}$$

$$Q = 7.2 \times 10^4 \text{ C}$$

Solve for  $\Delta t$  first

$$I\Delta t = \frac{Q}{\Delta t} \Delta t$$

$$Q = (20 \text{ A})(3600 \text{ s})$$

$$Q = 7.2 \times 10^4 \text{ C}$$

The total charge that will pass through the wire in one hour is  $7.2 \times 10^4 \text{ C}$ .

**Validate**

The answer is in coulombs, which is the correct unit for charge. The potential difference was not needed to solve the problem.

**10. Frame the Problem**

- The cellular phone battery draws a current through it.
- Charge, current, and time are all related.

**Identify the Goal**

To find the amount of current that the battery draws

**Variables and Constants**

Involvement in the Problem	Known	Unknown
$I$	$\Delta t = 0.25 \text{ h}$	$I$
$Q$	$Q = 2.5 \times 10^3 \text{ C}$	
$\Delta t$		

**Strategy**

Convert time to SI units.

Use the definition for current.

Divide and round up.

Since  $1 \frac{\text{C}}{\text{s}}$  is equivalent to 1 A, thus

The cellular phone battery draws 2.8 A of current during recharging.

**Calculations**

$$0.25 \text{ h} \left( \frac{60 \text{ min}}{\text{h}} \right) \left( \frac{60 \text{ s}}{\text{min}} \right) = 900 \text{ s}$$

$$I = \frac{Q}{\Delta t}$$

$$I = \frac{2.5 \times 10^3 \text{ C}}{900 \text{ s}}$$

$$I = 2.8 \frac{\text{C}}{\text{s}}$$

$$I = 2.8 \text{ A}$$

**Validate**

The answer is in amperes, which is the correct unit for current.

**11. Frame the Problem**

- The lights consume electric energy.
- Power, time, and electric energy are all related.

**Identify the Goal**

To find the electric energy consumed

**Variables and Constants**

Involvement in the Problem	Known	Unknown
$P_{\text{tot}}$	$\Delta t = 16 \text{ h}$	$P_{\text{tot}}$
$V$	$V = 240 \text{ V}$	$\Delta E_Q$
$\Delta t$	$P = 40 \text{ W}$	
$\Delta E_Q$	$N_{\text{lights}} = 200$	
$P$		
$N_{\text{lights}}$		

(Note:  $P_{\text{tot}}$  refers to the total power and  $N_{\text{lights}}$  refers to the number of lights)

**Strategy**

Convert time to SI units.

Find the total power.

**Calculations**

$$16 \text{ h} \left( \frac{60 \text{ min}}{\text{h}} \right) \left( \frac{60 \text{ s}}{\text{min}} \right) = 5.74 \times 10^4 \text{ s}$$

$$P_{\text{tot}} = (N_{\text{lights}})(P)$$

$$P_{\text{tot}} = (200)(40 \text{ W})$$

$$P_{\text{tot}} = 8000 \text{ W}$$



Use the definition of power to obtain the electric energy consumed.

$$P_{\text{tot}} = \frac{\Delta E_Q}{\Delta t}$$

Substitute first

$$(8000 \text{ W})(5.76 \times 10^4 \text{ s})$$

$$= \frac{\Delta E_Q}{(5.76 \times 10^4 \text{ s})} 5.76 \times 10^4 \text{ s}$$

$$\Delta E_Q = (5.76 \times 10^4 \text{ s})(8000 \text{ W})$$

Solve for  $\Delta E_Q$  first

$$P_{\text{tot}} \Delta t = \frac{\Delta E_Q}{\Delta t} \Delta t$$

$$\Delta E_Q = (5.76 \times 10^4 \text{ s})(8000 \text{ W})$$

Since 1 s·W is equivalent to 1 J, thus

$$\Delta E_Q = 4.6 \times 10^8 \text{ J}$$

The energy consumed is  $4.6 \times 10^8 \text{ J}$ .

**Validate**

The answer is in joules, which is the correct unit for energy. The potential difference was not needed to solve the problem.

**Solutions for Practice Problems**

**Student Textbook page 618**

**12. Frame the Problem**

- When elementary charges pass a point in a circuit there is current.
- If you know the time it took for a number of elementary charges to pass that point, you can calculate the current.

**Identify the Goal**

To calculate the current

**Variables and Constants**

Involved in the Problem	Known	Implied	Unknown
$I$	$N = 2.85 \times 10^{20}$	$e = 1.60 \times 10^{-19} \text{ C}$	$I$
$N$	$\Delta t = 5.70 \text{ min}$		$Q$
$e$			
$\Delta t$			
$Q$			

**Strategy**

Use the relationship between amount of charge and elementary charge.

Multiply

Convert time to SI units.

Use the definition for current.

Divide

Since  $1 \frac{\text{C}}{\text{s}}$  is equivalent to 1 A, thus

The current is 0.133 A.

**Calculations**

$$Q = Ne$$

$$Q = (2.85 \times 10^{20})(1.60 \times 10^{-19} \text{ C})$$

$$Q = 45.6 \text{ C}$$

$$5.70 \text{ min} \frac{60 \text{ s}}{\text{min}} = 342 \text{ s}$$

$$I = \frac{Q}{\Delta t}$$

$$I = \frac{45.6 \text{ C}}{342 \text{ s}}$$

$$I = 0.133 \text{ A}$$

**Validate**

The answer is in amperes, which is the correct unit for current.

**13. (a) Frame the Problem**

- The battery does a known amount of work at a known potential difference by moving an unknown amount of charge through a circuit in a known amount of time.
- Potential difference, work, and charge are all related.
- Current, charge, and time are all related.

**Identify the Goal**

To determine the current through the battery

**Variables and Constants**

**Involved in the Problem**

$I$

$\Delta E_Q$

$W$

$V$

$\Delta t$

$Q$

**Known**

$\Delta t = 360.0 \text{ s}$

$W = 5.40 \times 10^4 \text{ J}$

$V = 16.0 \text{ V}$

**Unknown**

$I$

$\Delta E_Q$

$Q$

**Strategy**

The amount of work done is equal to the potential energy.

Use the expression for potential difference to find the amount of charge.

**Calculations**

$$W = \Delta E_Q$$

$$W = 5.40 \times 10^4 \text{ J}$$

$$\Delta E_Q = 5.40 \times 10^4 \text{ J}$$

$$V = \frac{\Delta E_Q}{Q}$$

Substitute first

$$(16.0 \text{ V})Q = \frac{5.40 \times 10^4 \text{ J}}{Q}$$

$$\frac{(16.0 \text{ V})Q}{16.0 \text{ V}} = \frac{5.40 \times 10^4 \text{ J}}{16.0 \text{ V}}$$

$$Q = \frac{5.40 \times 10^4 \text{ J}}{16.0 \text{ V}}$$

$$Q = 3375 \text{ C}$$

$$Q = 3380 \text{ C}$$

$$I = \frac{Q}{\Delta t}$$

$$I = \frac{3380 \text{ C}}{360.0 \text{ s}}$$

$$I = 9.38 \text{ A}$$

Solve for  $Q$  first

$$VQ = \frac{\Delta E_Q}{Q}$$

$$\frac{VQ}{V} = \frac{\Delta E_Q}{V}$$

$$Q = \frac{5.40 \times 10^4 \text{ J}}{16.0 \text{ V}}$$

Since  $1 \frac{\text{J}}{\text{V}}$  is equivalent to 1 C, therefore

Round up

Use the definition for current.

Divide

Since  $1 \frac{\text{C}}{\text{s}}$  is equivalent to 1 A,

The current through the battery is 9.38 A.

**Validate**

The answer is in amperes, which is the correct unit for current.

**(b) Frame the Problem**

- When elementary charges pass a point in a circuit there is current.
- If you know the amount of charge that passes through the battery, you can use this magnitude to find the number of elementary charges (electrons).

**Identify the Goal**

The number ( $N$ ) of elementary charges (electrons) passing through the bulb

**Variables and Constants**

Involvement in the Problem	Known	Implied	Unknown
$N$	$Q = 3380 \text{ C}$	$e = 1.6 \times 10^{-19} \text{ C}$	$N$
$e$			
$Q$			

**Strategy**

Use the relationship between amount of charge and the elementary charge to find the number of electrons.

**Calculations**

$$Q = Ne$$

Substitute first

$$3380 \text{ C} = N(1.60 \times 10^{-19} \text{ C})$$

$$\frac{3380 \text{ C}}{1.60 \times 10^{-19} \text{ C}} = \frac{N(1.60 \times 10^{-19} \text{ C})}{1.60 \times 10^{-19} \text{ C}}$$

$$N = 2.11 \times 10^{22}$$

Solve for  $N$  first

$$\frac{Q}{e} = \frac{Ne}{e}$$

$$N = \frac{3380 \text{ C}}{1.60 \times 10^{-19} \text{ C}}$$

$$N = 2.11 \times 10^{22}$$

The number of elementary charges is  $2.11 \times 10^{22}$ .

**Validate**

The units cancel to give a pure number, as they should.

**14. Frame the Problem**

- When elementary charges pass a point in a circuit there is current.
- If you know the current at that point and the time it took to pass, you can calculate the number of elementary charges.

**Identify the Goal**

The number ( $N$ ) of elementary charges that pass through a point in the circuit

**Variables and Constants**

Involvement in the Problem	Known	Implied	Unknown
$I$	$I = 3.50 \text{ A}$	$e = 1.6 \times 10^{-19} \text{ C}$	$N$
$N$	$\Delta t = 24.0 \text{ s}$		$Q$
$e$			
$\Delta t$			
$Q$			

**Strategy**

Use the definition for current to solve for the amount of charge.

**Calculations**

$$I = \frac{Q}{\Delta t}$$

Substitute first

$$(3.50 \text{ A})(24.0 \text{ s}) = \frac{Q}{24.0 \text{ s}}(24.0 \text{ s})$$

$$Q = (3.50 \text{ A})(24.0 \text{ s})$$

$$Q = 84.0 \text{ C}$$

$$Q = Ne$$

Solve for  $Q$  first

$$I\Delta t = \frac{Q}{\Delta t}\Delta t$$

$$Q = (3.50 \text{ A})(24.0 \text{ s})$$

Since  $1 \text{ A}\cdot\text{s}$ , thus

Use the relationship between amount of

charge and elementary charge to find the number of electrons.

Substitute first

$$84.0 \text{ C} = N(1.60 \times 10^{-19} \text{ C})$$

$$\frac{84.0 \text{ C}}{1.60 \times 10^{-19} \text{ C}} = \frac{N(1.60 \times 10^{-19} \text{ C})}{1.60 \times 10^{-19} \text{ C}}$$

$$N = 5.25 \times 10^{20}$$

Solve for  $N$  first

$$\frac{Q}{e} = \frac{Ne}{e}$$

$$N = \frac{84.0 \text{ C}}{1.60 \times 10^{-19} \text{ C}}$$

$$N = 5.25 \times 10^{20}$$

The number of elementary charges is  $5.25 \times 10^{20}$ .

**Validate**

The units cancel out to yield a pure number, which is correct.

**15. (a) Frame the Problem**

- When elementary charges pass a point in a circuit there is current.
- If you know the time it took for a quantity of elementary charges to pass that point you can calculate the current.

**Identify the Goal**

To calculate the current

**Variables and Constants**

Involved in the Problem	Known	Implied	Unknown
$I$	$N = 2.5 \times 10^{20}$	$e = 1.6 \times 10^{-19} \text{ C}$	$I$
$N$	$\Delta t = 5.70 \text{ min}$		$Q$
$e$			
$\Delta t$			
$Q$			

**Strategy**

Use the relationship between amount of charge and elementary charge.

Multiply

Use the definition for current.

Divide

Since  $1 \frac{\text{C}}{\text{s}}$  is equivalent to 1 A, thus

The current is 3.3 A.

**Calculations**

$$Q = Ne$$

$$Q = (2.5 \times 10^{20})(1.60 \times 10^{-19} \text{ C})$$

$$Q = 40 \text{ C}$$

$$I = \frac{Q}{\Delta t}$$

$$I = \frac{40 \text{ C}}{12 \text{ s}}$$

$$I = 3.3 \text{ A}$$

**Validate**

The answer is in amperes, which is the correct unit for current.

**(b) Frame the Problem**

- The potential difference drives a current through the circuit.
- The amount of work done by the current is the same as the change in the potential energy of the charges as they move through the circuit.
- The expressions that define potential difference and work done apply to this problem.

**Identify the Goal**

To find the potential difference of the battery

**Variables and Constants**

Involved in the Problem	Known	Unknown
$\Delta E_Q$	$W = 68 \text{ J}$	$\Delta E_Q$
$W$	$Q = 40 \text{ C}$	$V$
$V$		
$Q$		

**Strategy**

The amount of work done is equal to the potential energy.

Use the expression for potential difference.

Substitute in the values.

Divide

Since  $1 \frac{\text{J}}{\text{C}}$  is equivalent to 1 V, thus

The potential difference is 1.7 V.

**Calculations**

$$W = \Delta E_Q$$

$$W = 68 \text{ J}$$

$$\Delta E_Q = 68 \text{ J}$$

$$V = \frac{\Delta E_Q}{Q}$$

$$V = \frac{68 \text{ J}}{40 \text{ C}}$$

$$V = 1.7 \frac{\text{J}}{\text{C}}$$

$$V = 1.7 \text{ V}$$

**Validate**

The answer is in volts, which is the correct unit for potential difference.

**Solutions for Practice Problems**

**Student Textbook page 626**

**16. Frame the Problem**

- The electrical resistance of a conductor depends on its length, its cross-sectional area, the resistivity of the conducting material, and the temperature.
- These variables are related by the equation for resistance of a conductor.
- The resistivity of aluminum at 20°C is listed in Table 13.1 of the textbook.

**Identify the Goal**

Resistance,  $R$ , of the aluminum conductor

**Variables and Constants**

Involved in the Problem	Known	Implied	Unknown
$R$	$d = 2.0 \text{ mm}$	$\rho = 2.7 \times 10^{-8} \Omega \cdot \text{m}$	$R$
$L$	$L = 250 \text{ m}$		
$d$			
$A$			
$\rho$			

**Strategy**

Use the equation relating resistance to resistivity and dimensions of the conductor.

Convert time to SI units. (All others are in SI units.)

**Calculations**

$$R = \rho \frac{L}{A}$$

$$2.0 \text{ mm} \frac{\text{m}}{1000 \text{ mm}} = 2.0 \times 10^{-3} \text{ m}$$

Find the cross-sectional area from the diameter.

$$A = \pi r^2$$

$$r = \frac{d}{2}$$

$$r = \frac{2.0 \times 10^{-3} \text{ m}}{2} = 1.0 \times 10^{-3} \text{ m}$$

Values are all known, so substitute into the equation for resistance and round up.

$$A = \pi(1.0 \times 10^{-3} \text{ m})^2$$

$$A = 3.1 \times 10^{-6} \text{ m}^2$$

$$R = (2.7 \times 10^{-8} \Omega \cdot \text{m}) \frac{250 \text{ m}}{3.1 \times 10^{-6} \text{ m}^2}$$

$$R = 2.15 \frac{\Omega \cdot \text{m} \cdot \text{m}}{\text{m}^2}$$

$$R = 2.2 \Omega$$

The resistance is 2.2 Ω.

**Validate**

The units combined to give ohms, which is correct.

**17. Frame the Problem**

- The electrical resistance of a conductor depends on its length, its cross-sectional area, the resistivity of the conducting material, and the temperature.
- These variables are related by the equation for resistance of a conductor.
- The diameter of the wire is listed in p. 624 of the textbook.
- The resistivity of Nichrome™ at 20°C is listed in Table 13.1 of the textbook.

**Identify the Goal**

The length, *L*, of the Nichrome wire

**Variables and Constants**

Involved in the Problem	Known	Implied	Unknown
<i>R</i>	<i>R</i> = 5.0 Ω	$\rho = 100 \times 10^{-8} \Omega \cdot \text{m}$	<i>L</i>
<i>L</i>		<i>d</i> = 1.02 mm	<i>A</i>
<i>d</i>			
<i>A</i>			
$\rho$			

**Strategy**

Use the equation relating resistance to resistivity and dimensions of the conductor.

Convert to SI units. (All others are in SI units.)

Find the cross-sectional area from the diameter.

Solve for the length of the wire.

**Calculations**

$$R = \rho \frac{L}{A}$$

$$1.02 \frac{\text{mm}}{1000 \frac{\text{mm}}{\text{m}}} = 1.02 \times 10^{-3} \text{ m}$$

$$A = \pi r^2$$

$$r = \frac{d}{2}$$

$$r = \frac{1.02 \times 10^{-3} \text{ m}}{2} = 0.51 \times 10^{-3} \text{ m}$$

$$A = \pi(0.51 \times 10^{-3} \text{ m})^2$$

$$A = 8.17 \times 10^{-7} \text{ m}^2$$

Substitute first

$$500 \Omega = (100 \times 10^{-8} \Omega \cdot \text{m}) \frac{L}{8.17 \times 10^{-7} \text{ m}^2}$$

$$500 \Omega \frac{8.17 \times 10^{-7} \text{ m}^2}{100 \times 10^{-8} \Omega \cdot \text{m}}$$

$$= (100 \times 10^{-8} \Omega \cdot \text{m}) \frac{L}{8.17 \times 10^{-7} \text{ m}^2} \frac{8.17 \times 10^{-7} \text{ m}^2}{100 \times 10^{-8} \Omega \cdot \text{m}}$$

$$L = 500 \Omega \frac{8.17 \times 10^{-7} \text{ m}^2}{100 \times 10^{-8} \Omega \cdot \text{m}}$$

$$L = 4.08 \text{ m}$$

Solve for  $L$  first

$$R \frac{A}{\rho} = \rho \frac{L}{A} \frac{A}{\rho}$$

$$L = 500 \Omega \frac{8.17 \times 10^{-7} \text{ m}^2}{100 \times 10^{-8} \Omega \cdot \text{m}}$$

$$L = 4.08 \text{ m}$$

The length of the wire is 4.08 m.

### Validate

The units combined to give meters, which is correct.

### 18. Frame the Problem

- The electric resistance of a 100 W tungsten filament depends on its length, its cross-sectional area, the resistivity of the conducting material, and the temperature.
- These variables are related by the equation for resistance of a conductor.
- The resistivity of tungsten at 20°C is listed in Table 13.1 of the textbook.

### Identify the Goal

The radius,  $r$ , of the tungsten wire

### Variables and Constants

Involved in the Problem	Known	Implied	Unknown
$R$	$R = 144 \Omega$	$\rho = 5.6 \times 10^{-8} \Omega \cdot \text{m}$	$r$
$L$	$L = 2.0 \text{ cm}$		$A$
$r$	$P = 100 \text{ W}$		
$d$			
$A$			
$\rho$			

### Strategy

Use the equation relating resistance to resistivity and dimensions of the conductor.

Convert time to SI units. (All others are in SI units.)

Solve for the area of the wire.

### Calculations

$$R = \rho \frac{L}{A}$$

$$2.0 \text{ cm} \frac{\text{m}}{100 \text{ cm}} = 2.0 \times 10^{-2} \text{ m}$$

Substitute first

$$144 \Omega \cdot A = (5.6 \times 10^{-8} \Omega \cdot \text{m}) \frac{2.0 \times 10^{-2} \text{ m} \cdot A}{A}$$

$$144 \Omega \cdot \frac{A}{144 \Omega} = (5.6 \times 10^{-8} \Omega \cdot \text{m}) \frac{2.0 \times 10^{-2} \text{ m}}{144 \Omega}$$

$$A = (5.6 \times 10^{-8} \Omega \cdot \text{m}) \frac{2.0 \times 10^{-2} \text{ m}}{144 \Omega}$$

$$A = 7.8 \times 10^{-12} \text{ m}^2$$

Solve for  $A$  first

$$RA = \rho \frac{L}{A} A$$

$$\frac{R}{R} A = \rho \frac{L}{R}$$

$$A = 5.6 \times 10^{-8} \Omega \cdot \text{m} \frac{2.0 \times 10^{-2} \text{ m}}{144 \Omega}$$

$$A = 7.8 \times 10^{-12} \text{ m}^2$$

Find the radius of the filament.

Substitute first

$$7.8 \times 10^{-12} \text{ m}^2 = \pi r^2$$

$$\frac{7.8 \times 10^{-12} \text{ m}^2}{\pi} = r^2 \frac{\pi}{\pi}$$

$$r = \sqrt{\frac{7.8 \times 10^{-12} \text{ m}^2}{\pi}}$$

$$r = 1.6 \times 10^{-6} \text{ m}$$

Solve for  $r$  first

$$A = \pi r^2$$

$$\frac{A}{\pi} = r^2 \frac{\pi}{\pi}$$

$$r = \sqrt{\frac{7.8 \times 10^{-12} \text{ m}^2}{\pi}}$$

$$r = 1.6 \times 10^{-6} \text{ m}$$

The radius of the tungsten wire is  $1.6 \times 10^{-6} \text{ m}$ .

**Validate**

The units combined to give meters, which is correct. Also notice that the radius is very small which is what we would want so that it has a large resistance. Finally, note that the power,  $P$ , was not needed in the problem.

**19. Frame the Problem**

- The electrical resistance of a conductor depends on its length, its cross-sectional area, the resistivity of the conducting material, and the temperature.
- These variables are related by the equation for resistance of a conductor.
- The resistivity of aluminum at  $20^\circ\text{C}$  is listed in Table 13.1 of the textbook.

**Identify the Goal**

Resistance,  $R$ , of the aluminum conductor

**Variables and Constants**

Involved in the Problem	Known	Implied	Unknown
$R$	$L = 250 \text{ cm}$	$\rho = 2.7 \times 10^{-8} \Omega \cdot \text{m}$	$R$
$L$		$d = 1.63 \text{ mm}$	$A$
$d$			
$A$			
$\rho$			

**Strategy**

Use the equation relating resistance to resistivity and dimensions of the conductor.

Convert time to SI units. (All others are in SI units.)

**Calculations**

$$R = \rho \frac{L}{A}$$

$$1.63 \frac{\text{mm}}{1000 \frac{\text{mm}}{\text{m}}} = 1.63 \times 10^{-3} \text{ m}$$



Find the cross-sectional area from the diameter.

$$A = \pi r^2$$

$$r = \frac{d}{2}$$

$$r = \frac{1.63 \times 10^{-3} \text{ m}}{2} = 8.15 \times 10^{-4} \text{ m}$$

$$A = \pi(8.15 \times 10^{-4} \text{ m})^2$$

$$A = 2.08 \times 10^{-6} \text{ m}^2$$

Values are all known, so substitute into the equation for resistance.

$$R = (2.7 \times 10^{-8} \Omega \cdot \text{m}) \frac{35 \text{ m}}{2.08 \times 10^{-6} \text{ m}^2}$$

$$R = 0.45 \frac{\Omega \cdot \text{m} \cdot \text{m}}{\text{m}^2}$$

$$R = 0.45 \Omega$$

The resistance is  $0.45 \Omega$ .

**Validate**

The units combined to give ohms, which is correct.

**20. Frame the Problem**

- The electrical resistance of a small carbon rod depends on its length, its cross-sectional area, the resistivity of the conducting material, and the temperature.
- These variables are related by the equation for resistance of a conductor.
- The resistivity of carbon at  $20^\circ\text{C}$  is listed in Table 13.1 of the textbook.

**Identify the Goal**

The width,  $w$ , of the square carbon rod

**Variables and Constants**

Involved in the Problem	Known	Implied	Unknown
$R$	$R = 140 \Omega$	$\rho = 3500 \times 10^{-8} \Omega \cdot \text{m}$	$w$
$L$	$L = 24 \text{ m}$		$A$
$w$			
$A$			
$\rho$			

**Strategy**

Use the equation relating resistance to resistivity and dimensions of the conductor.

Solve for the area of the wire.

**Calculations**

$$R = \rho \frac{L}{A}$$

Substitute first

$$140 \Omega \cdot A = (3500 \times 10^{-8} \Omega \cdot \text{m}) \frac{24 \text{ m}}{A}$$

$$140 \Omega \cdot \frac{A}{140 \Omega} = (3500 \times 10^{-8} \Omega \cdot \text{m}) \frac{24 \text{ m}}{140 \Omega}$$

$$A = (3500 \times 10^{-8} \Omega \cdot \text{m}) \frac{24 \text{ m}}{140 \Omega}$$

$$A = 6.0 \times 10^{-6} \text{ m}^2$$

Solve for A first

$$RA = \rho \frac{L}{A} A$$

$$\frac{R}{R} A = \rho \frac{L}{R}$$

$$A = 3500 \times 10^{-8} \Omega \cdot \text{m} \frac{24 \text{ m}}{140 \Omega}$$

$$A = 6.0 \times 10^{-6} \text{ m}^2$$

Find the width of the carbon square.

Substitute first

$$6.0 \times 10^{-6} \text{ m}^2 = w^2$$

$$w = \sqrt{6.0 \times 10^{-6} \text{ m}^2}$$

$$w = 2.4 \times 10^{-3} \text{ m}$$

Solve for  $w$  first

$$A = w^2$$

$$w = \sqrt{6.0 \times 10^{-6} \text{ m}^2}$$

$$w = 2.4 \times 10^{-3} \text{ m}$$

The width of the square carbon rod is  $2.4 \times 10^{-3} \text{ m}$  or 2.4 mm.

### Validate

The units combined to give meters, which is correct.

## Solutions for Practice Problems

### Student Textbook page 632

#### 21. Frame the Problem

- The power supply creates a potential difference that provides energy to cause a current to flow in the electric kettle.
- You can find the resistance of the element by Ohm's law.

#### Identify the Goal

Resistance,  $R$ , of the element

#### Variables and Constants

##### Involved in the Problem

$R$

$I$

$V$

##### Known

$$I = 7.5 \text{ A}$$

$$V = 120 \text{ V}$$

##### Unknown

$R$

#### Strategy

Apply Ohm's law.

#### Calculations

$$V = IR$$

Substitute first

$$120 \text{ V} = (7.5 \text{ A})R$$

$$120 \text{ V} \cdot \frac{1}{7.5 \text{ A}} = (7.5 \text{ A}) \frac{R}{7.5 \text{ A}}$$

$$R = \frac{120 \text{ V}}{7.5 \text{ A}}$$

$$R = 16 \ \Omega$$

Solve for  $R$  first

$$V = IR$$

$$V \cdot \frac{1}{I} = I \frac{R}{I}$$

$$R = \frac{120 \text{ V}}{7.5 \text{ A}}$$

$$R = 16 \ \Omega$$

The resistance is  $16 \ \Omega$ .

### Validate

The units combined to give ohms, which is correct.

#### 22. Frame the Problem

- The toaster has a potential difference that provides energy to cause a current to flow through it.
- You can find the current through the toaster by Ohm's law.

#### Identify the Goal

The current,  $I$ , through the toaster

**Variables and Constants****Involved in the Problem** $R$  $I$  $V$ **Known**

$R = 9.60 \Omega$

$V = 120 \text{ V}$

**Unknown** $I$ **Strategy**

Apply Ohm's law.

**Calculations**

$V = IR$

Substitute first

$120 \text{ V} = I(9.60 \Omega)$

$120 \text{ V} \cdot \frac{1}{9.60 \Omega} = (9.60 \Omega) \frac{1}{9.60 \Omega}$

$I = \frac{120 \text{ V}}{9.60 \Omega}$

$I = 12.5 \text{ A}$

Solve for  $I$  first

$V = IR$

$V \cdot \frac{1}{R} = R \frac{1}{R}$

$I = \frac{120 \text{ V}}{9.60 \Omega}$

$I = 12.5 \text{ A}$

The current is 12.5 A.

**Validate**

The units combined to give amperes, which is correct.

**23. Frame the Problem**

- The light bulb has a potential difference that provides energy to cause a current to flow through it.
- You can find the operating potential difference by Ohm's law.

**Identify the Goal**The operating potential difference,  $V$ **Variables and Constants****Involved in the Problem** $R$  $I$  $V$ **Known**

$R = 36 \Omega$

$I = 140 \text{ mA}$

**Unknown** $V$ **Strategy**

Apply Ohm's law.

**Calculations**

$V = IR$

$V = (140 \text{ mA})(36 \Omega)$

$V = 5.0 \text{ V}$

The potential difference is 5.0 V.

**Validate**

The units combined to give volts, which is correct.

**24. Frame the Problem**

- The light bulb in the tail-light of an automobile has a potential difference that provides energy to cause a current to flow through it.
- You can find the current through the tail-light by Ohm's law.
- You can find the quantity of charge that passes through the bulb by the definition of current.
- The work done transforms chemical potential energy into electric potential energy. Thus, the electric potential energy is equal to the amount of work done.
- The expression that defines potential difference applies to this problem.

**Identify the Goal**

- (a) The quantity of charge,  $Q$ , through the bulb
- (b) The amount of work that has been done on the charge.

**Variables and Constants**

Involved in the Problem	Known	Unknown
$R$	$R = 5.8 \Omega$	$I$
$I$	$V = 12 \text{ V}$	$Q$
$V$	$\Delta t = 8.0 \text{ min}$	$W$
$\Delta t$	$V = 12 \text{ V}$	$\Delta E_Q$
$Q$		
$W$		
$\Delta E_Q$		
$V$		

**Strategy**

Apply Ohm's law.

**Calculations**

$$V = IR$$

Substitute first

$$12 \text{ V} = I(5.8 \Omega)$$

$$12 \text{ V} \cdot \frac{1}{5.8 \Omega} = (5.8 \text{ A}) \frac{I}{12 \Omega}$$

$$I = \frac{12 \text{ V}}{5.8 \Omega}$$

$$I = 2.07 \text{ A}$$

$$I = \frac{Q}{\Delta t}$$

Solve for  $I$  first

$$V = IR$$

$$V \cdot \frac{1}{R} = R \frac{I}{R}$$

$$I = \frac{12 \text{ V}}{5.8 \Omega}$$

$$I = 2.07 \text{ A}$$

Use the expression for the electric current to solve for the charge and use the fact that A·s is equivalent to C.

Substitute first

$$(2.07 \text{ A})(480 \text{ s})$$

$$= \frac{Q}{480 \text{ s}}(480 \text{ s})$$

$$Q = (2.07 \text{ A})(480 \text{ s})$$

$$Q = 990 \text{ C}$$

Solve for  $Q$  first

$$I\Delta t = \frac{Q}{\Delta t}\Delta t$$

$$Q = (2.07 \text{ A})(480 \text{ s})$$

$$Q = 990 \text{ C}$$

- (a) The charge is 990 C and the current is 2.0 A.

**Strategy**

Use the expression for the potential difference.

Solve for  $\Delta E_Q$ ; V·C is 1 J.

**Calculations**

$$V = \frac{\Delta E_Q}{Q}$$

Substitute first

$$12 \text{ V} = \frac{\Delta E_Q}{990 \text{ C}}$$

$$(12 \text{ V})(990 \text{ C})$$

$$= \frac{\Delta E_Q}{990 \text{ C}}(12 \text{ C})$$

$$\Delta E_Q = 1.2 \times 10^4 \text{ J}$$

Solve for  $\Delta E_Q$  first

$$VQ = \frac{\Delta E_Q}{Q}Q$$

$$\Delta E_Q = (12 \text{ V})(990 \text{ J})$$

$$\Delta E_Q = 1.2 \times 10^4 \text{ J}$$

The amount of work done is equal to the potential energy.

1 V·C is equivalent to 1 J, thus

$$W = \Delta E_Q$$

$$W = 1.2 \times 10^4 \text{ J}$$

- (b) The amount of work done on the charge is  $1.2 \times 10^4 \text{ J}$ .

**Validate**

The units combined to give coulombs for the charge and joules for the work, which is correct.

**25. Frame the Problem**

- The electric potential energy is equal to the amount of work done.
- The expression that defines potential difference applies to this problem.
- From the charge you can obtain the current.
- From the current you can obtain the resistance.

**Identify the Goal**

The resistance of the iron

**Variables and Constants**

Involved in the Problem	Known	Unknown
$W$	$W = 3.35 \times 10^5 \text{ J}$	$Q$
$\Delta E_Q$	$V = 120 \text{ V}$	$R$
$V$	$\Delta t = 4.50 \text{ min}$	$I$
$Q$		$\Delta E_Q$
$I$		
$R$		
$\Delta t$		

**Strategy**

Use the expression for the potential difference.

The amount of work done is equal to the potential energy.

Solve for the charge.

$1 \frac{\text{J}}{\text{V}}$  is equivalent to 1 C, thus

Convert time to SI units.

Use the expression for the electric current to solve for the current.

Substitute and divide.

$1 \frac{\text{C}}{\text{s}}$  is equivalent to 1 A, thus

Apply Ohm's law.

**Calculations**

$$V = \frac{\Delta E_Q}{Q}$$

$$W = \Delta E_Q$$

$$W = 3.35 \times 10^5 \text{ J}$$

Substitute first

$$(120 \text{ V})Q = \frac{3.35 \times 10^5 \text{ J}}{Q}$$

$$\frac{(120 \text{ V})Q}{120 \text{ V}} = \frac{3.35 \times 10^5 \text{ J}}{120 \text{ V}}$$

$$Q = \frac{3.35 \times 10^5 \text{ J}}{120 \text{ V}}$$

Solve for  $Q$  first

$$VQ = \frac{\Delta E_Q}{Q}$$

$$\frac{VQ}{V} = \frac{\Delta E_Q}{V}$$

$$Q = \frac{3.35 \times 10^5 \text{ J}}{120 \text{ V}}$$

$$Q = 2.80 \times 10^3 \text{ C}$$

$$4.50 \text{ min} \frac{60 \text{ s}}{\text{min}} = 270 \text{ s}$$

$$I = \frac{Q}{\Delta t}$$

$$I = \frac{2.80 \times 10^3 \text{ C}}{270 \text{ s}}$$

$$I = 10.3 \text{ A}$$

$$V = IR$$

Substitute first

$$120 \text{ V} = (10.3 \text{ A})R$$

$$120 \text{ V} \cdot \frac{1}{10.3 \text{ A}} = (10.3 \text{ A}) \frac{R}{10.3 \text{ A}}$$

$$R = \frac{120 \text{ V}}{10.3 \text{ A}}$$

$$R = 11.6 \Omega$$

Solve for  $R$  first

$$V = IR$$

$$V \cdot \frac{1}{I} = \cancel{I} \frac{R}{\cancel{I}}$$

$$R = \frac{120 \text{ V}}{10.3 \text{ A}}$$

$$R = 11.6 \Omega$$

The resistance is  $11.6 \Omega$ .

Alternative strategy: use two formulas for power,  $P = \frac{\Delta E_Q}{\Delta t}$  and  $P = \frac{V^2}{R}$ . Since  $W = \Delta E_Q$ , these formulas combine to give  $\frac{W}{\Delta t} = \frac{V^2}{R}$ . Substitute and solve for  $R$ , or rearrange to solve for  $R$  first.

### Validate

The units combined to give ohms, which is correct.

## 26. Frame the Problem

- The electrical potential energy is equal to the amount of work done.
- The expression that defines potential difference applies to this problem.
- From Ohm's law you can obtain the current.
- From the definition of current you can obtain the time.

### Identify the Goal

The time to produce  $4.32 \times 10^5 \text{ J}$  of thermal energy

### Variables and Constants

Involved in the Problem	Known	Unknown
$W$	$W = 4.32 \times 10^5 \text{ J}$	$Q$
$\Delta E_Q$	$V = 240 \text{ V}$	$\Delta t$
$V$	$R = 60.0 \Omega$	$I$
$Q$		$\Delta E_Q$
$I$		
$R$		
$\Delta t$		

### Strategy

Use the expression for the potential difference.

The amount of work done is equal to the potential energy.

Solve for the charge.

### Calculations

$$V = \frac{\Delta E_Q}{Q}$$

$$W = \Delta E_Q$$

$$\Delta E_Q = 4.32 \times 10^5 \text{ J}$$

Substitute first

$$(240 \text{ V})Q = \frac{4.32 \times 10^5 \text{ J}}{Q}$$

$$\frac{(240 \text{ V})Q}{240 \text{ V}} = \frac{4.32 \times 10^5 \text{ J}}{240 \text{ V}}$$

$$Q = \frac{4.32 \times 10^5 \text{ J}}{120 \text{ V}}$$

Solve for  $Q$  first

$\frac{J}{V}$  is equivalent to 1 C, thus  
Apply Ohm's law.

$$\frac{W}{V} = \frac{\Delta E_Q}{Q} \cdot Q$$

$$\frac{W}{V} = \frac{\Delta E_Q}{V}$$

$$Q = \frac{4.32 \times 10^5 \text{ J}}{120 \text{ V}}$$

$$Q = 1800 \text{ C}$$

$$V = \frac{I}{R}$$

Substitute first

$$240 \text{ V} = I(60.0 \ \Omega)$$

$$240 \text{ V} \cdot \frac{1}{60.0 \ \Omega} = (60.0 \text{ A}) \frac{I}{12 \ \Omega}$$

$$I = \frac{240 \text{ V}}{60.0 \ \Omega}$$

$$I = 4.00 \text{ V}$$

Solve for  $I$  first

$$V = IR$$

$$V \cdot \frac{1}{R} = R \frac{I}{R}$$

$$I = \frac{240 \text{ V}}{60.0 \ \Omega}$$

$$I = 4.00 \text{ A}$$

$$I = \frac{Q}{\Delta t}$$

Use the expression for the electric current to obtain the time.

Substitute first

$$(4.00 \text{ A})\Delta t = \frac{1800 \text{ C}}{\Delta t} \Delta t$$

$$\Delta t = \frac{1800 \text{ C}}{4.00 \text{ A}}$$

Solve for  $\Delta t$  first

$$I\Delta t = \frac{Q}{\Delta t} \Delta t$$

$$\frac{\Delta t}{\cancel{\Delta t}} I = \frac{Q}{I}$$

$$\Delta t = \frac{1800 \text{ C}}{4.00 \text{ A}}$$

$$\Delta t = 450 \text{ s}$$

$1 \frac{\text{C}}{\text{A}}$  is equivalent to 1 s.

It would take 450 s or  $450 \text{ s} \frac{1 \text{ min}}{60 \text{ s}} = 7.50 \text{ min}$  for the battery to do the amount of work.

### Validate

The units combined to give seconds, which is correct.

## Solutions for Practice Problems

### Student Textbook pages 637 and 638

#### 27. Frame the Problem

- Since all the resistors are in series, the formula for the equivalent resistance for a series circuit applies to the problem.
- Ohm's law applies to each individual circuit element.

#### Identify the Goal

The equivalent resistance,  $R_S$

The potential differences  $V_1$ ,  $V_2$ , and  $V_3$  across the  $15.0 \ \Omega$ ,  $24.0 \ \Omega$ , and  $36.0 \ \Omega$  resistances, respectively

The potential difference of the battery,  $V_S$

### Variables and Constants

Involved in the Problem		Known	Unknown
$R_1$	$V_1$	$I_1 = 2.2 \text{ A}$	$V_1$
$R_2$	$V_2$	$R_1 = 15.0 \ \Omega$	$V_2$
$R_S$	$V_3$	$R_2 = 24.0 \ \Omega$	$V_3$
$R_S$	$V_S$	$R_3 = 36.0 \ \Omega$	$V_S$
$I_1$			$I_2$
$I_2$			$I_3$
$I_3$			$I_S$
$I_S$			$R_S$

### Strategy

Since the circuit has only one closed loop the current is the same everywhere in the circuit.

Use Ohm's law, the current, and the resistance of each resistor to find the potential drop across each resistor.

(a) The potential drops are 33 V, 53 V, and 79 V, respectively.

### Strategy

Use the equation for resistance of a series circuit.

(b) The equivalent resistance for the four resistors in series is 75  $\Omega$ .

### Strategy

Use Ohm's law to find the potential difference of the battery.

(c) The potential difference of the battery is  $1.6 \leftrightarrow 10^2 \text{ V}$

### Validate

If you combine the potential differences across the three loads found in part (a), the sum of the potential differences should equal  $1.6 \leftrightarrow 10^2 \text{ V}$ .

$$V_1 + V_2 + V_3 = 33 \text{ V} + 53 \text{ V} + 79 \text{ V} = 1.6 \leftrightarrow 10^2 \text{ V}$$

## 28. Frame the Problem

- Since all the resistors are in series, the formula for the equivalent resistance of a series circuit applies to the problem.
- Ohm's law applies to each individual circuit element.

### Identify the Goal

The potential difference  $V_2$  across the 35.0  $\Omega$  resistance

The potential difference of the battery,  $V_S$

### Calculations

$$I_1 = I_2 = I_3 = I_S = 2.2 \text{ A}$$

$$V_1 = I_1 R_1 = (2.2 \text{ A})(15.0 \ \Omega) = 33 \text{ V}$$

$$V_2 = I_2 R_2 = (2.2 \text{ A})(24.0 \ \Omega) = 53 \text{ V}$$

$$V_3 = I_3 R_3 = (2.2 \text{ A})(36.0 \ \Omega) = 79 \text{ V}$$

### Calculations

$$R_S = R_1 + R_2 + R_3$$

$$= 15.0 \ \Omega + 24.0 \ \Omega + 36.0 \ \Omega$$

$$= 75 \ \Omega$$

### Calculations

$$V_S = I_S R_S$$

$$= (2.2 \text{ A})(75 \ \Omega)$$

$$= 1.6 \leftrightarrow 10^2 \text{ V}$$



**Variables and Constants**

Involved in the Problem		Known	Unknown
$R_1$	$V_1$	$V_1 = 65.0 \text{ V}$	$V_2$
$R_2$	$V_2$	$R_1 = 25.0 \ \Omega$	$I_1$
$R_S$	$V_S$	$R_2 = 35.0 \ \Omega$	$I_2$
$I_1$			$V_S$
$I_2$			$I_S$
$I_S$			$R_S$

**Strategy**

Find the current through the first resistor using Ohm's law.

**Calculations**

$$V_1 = I_1 R_1$$

Substitute first

$$65.0 \text{ V} = I_1(25.0 \ \Omega)$$

$$65.0 \text{ V} \cdot \frac{1}{25.0 \ \Omega} = (25.0 \ \Omega) \frac{I_1}{25.0 \ \Omega}$$

$$I_1 = \frac{65.0 \text{ V}}{25.0 \ \Omega}$$

$$I_1 = 2.60 \text{ A}$$

Solve for  $I_1$  first

$$V = I_1 R$$

$$V_S \frac{1}{R} = R \frac{I_1}{R}$$

$$I_1 = \frac{65.0 \text{ V}}{25.0 \ \Omega}$$

$$I_1 = 2.60 \text{ A}$$

$$I_1 = I_2 = I_3 = I_S = 2.60 \text{ A}$$

Since the circuit has only one closed loop the current is the same everywhere in the circuit.

Use Ohm's law, the current, and the resistance of  $35.0 \ \Omega$  resistor to find the potential drop across it.

**(a)** The potential drop is  $91.0 \text{ V}$ .

$$V_2 = I_2 R_2 = (2.60 \text{ A})(35.0 \ \Omega) = 91.0 \text{ V}$$

**Strategy**

Use the equation for resistance of a series circuit.

Use Ohm's law to find the potential difference of the battery.

**Calculations**

$$R_S = R_1 + R_2$$

$$= 25.0 \ \Omega + 35.0 \ \Omega$$

$$= 60.0 \ \Omega$$

$$V_S = I R_S$$

$$= (2.60 \text{ A})(60.0 \ \Omega)$$

$$= 1.56 \leftrightarrow 10^2 \text{ V}$$

**(b)** The potential drop of the battery is  $1.56 \leftrightarrow 10^2 \text{ V}$ .

**Validate**

If you combine the potential differences across the two loads, the sum of the potential differences should equal  $1.56 \leftrightarrow 10^2 \text{ V}$ .

$$V_1 + V_2 = 1.56 \leftrightarrow 10^2 \text{ V}$$

**29. Frame the Problem**

- Since all the resistors are in series, the formula for the equivalent resistance for a series circuit applies to the problem.
- Ohm's law applies to each individual circuit element.

**Identify the Goal**

The resistance  $R_2$  of the second load

**Variables and Constants**

Involved in the Problem		Known	Unknown
$R_1$	$V_1$	$V_1 = 40.0 \text{ V}$	$V_2$
$R_2$	$V_2$	$R_1 = 48.0 \ \Omega$	$I_1$
$R_S$	$V_S$	$V_S = 75.0 \text{ V}$	$I_2$
$I_1$			$R_2$
$I_2$			$I_S$
$I_S$			$R_S$

**Strategy**

Find the current through the first resistor using Ohm's law.

**Calculations**

$$V = I_1 R_1$$

Substitute first

$$40.0 \text{ V} = I_1(48.0 \ \Omega)$$

$$40.0 \text{ V} \cdot \frac{1}{48.0 \ \Omega} = (48.0 \ \Omega) \frac{I_1}{48.0 \ \Omega}$$

$$I_1 = \frac{40.0 \text{ V}}{48.0 \ \Omega}$$

$$I_1 = 0.833 \text{ A}$$

Solve for  $I$  first

$$V = I_1 R$$

$$V \cdot \frac{1}{R} = R \frac{I}{R}$$

$$I_1 = \frac{40.0 \text{ V}}{48.0 \ \Omega}$$

$$I_1 = 0.833 \text{ A}$$

$$I_1 = I_2 = I_3 = 0.833 \text{ A}$$

Since the circuit has only one closed loop the current is the same everywhere in the circuit.

Subtract the potential drop across the first load from the battery to obtain the potential drop across the second load.

$$\begin{aligned} V_2 &= V_S - V_1 \\ &= 75.0 \text{ V} - 40.0 \text{ V} \\ &= 35.0 \text{ V} \end{aligned}$$

Apply Ohm's law to find the resistance of the second load.

$$V_2 = I_2 R_2$$

Substitute first

$$35.0 \text{ V} = (0.833 \text{ A}) R_2$$

$$35.0 \text{ V} \cdot \frac{1}{0.833 \text{ A}} = (0.833 \text{ A}) \frac{R_2}{0.833 \text{ A}}$$

$$R_2 = \frac{35.0 \text{ V}}{0.833 \text{ A}}$$

$$R_2 = \frac{35.0 \text{ V}}{0.833 \text{ A}}$$

$$R_2 = 42.0 \ \Omega$$

Solve for  $R_2$  first

$$V_2 = I_2 R_2$$

$$V_2 \cdot \frac{1}{I_2} = \cancel{I_2} \frac{R_2}{\cancel{I_2}}$$

$$R_2 = \frac{35.0 \text{ V}}{0.833 \text{ A}}$$

$$R_2 = 42.0 \ \Omega$$

The resistance is  $42.0 \ \Omega$ .**Validate**

The units combined to give ohms, which is correct.

**30. Frame the Problem**

- Since all the resistors are in series, the formula for the equivalent resistance for a series circuit applies to the problem.
- Ohm's law applies to each individual circuit element.

**Identify the Goal**The resistance  $R_1$  of the first loadThe potential difference of the battery,  $V_S$ The equivalent resistance of the two loads,  $R_S$ **Variables and Constants**

Involved in the Problem		Known	Unknown
$R_1$	$V_1$	$I_1 = 7.00 \text{ A}$	$V_2$
$R_2$	$V_2$	$R_2 = 24.0 \ \Omega$	$I_1$
$R_S$	$V_S$	$V_1 = 56.0 \text{ V}$	$V_S$
$I_1$			$R_1$
$I_2$			$I_S$
$I_S$			$R_S$

**Strategy**

Since the circuit has only one closed loop the current is the same everywhere in the circuit.

Apply Ohm's law to find the resistance of the first load.

**Calculations**

$$I_1 = I_2 = I_S = 7.00 \text{ A}$$

$$V_1 = I_1 R_1$$

Substitute first

$$56.0 \text{ V} = (7.00 \text{ A})R$$

$$56.0 \text{ V} \cdot \frac{1}{7.00 \text{ A}} = (7.00 \text{ A}) \frac{R}{7.00 \text{ A}}$$

$$R_1 = \frac{56.0 \text{ V}}{7.00 \text{ A}}$$

$$R_1 = 8.00 \ \Omega$$

Solve for  $R_1$  first

$$V_1 = I_1 R_1$$

$$V_1 \cdot \frac{1}{I_1} = \cancel{I_1} \frac{R_1}{\cancel{I_1}}$$

$$R_1 = \frac{56.0 \text{ V}}{7.00 \text{ A}}$$

$$R_1 = 8.00 \ \Omega$$

**(a)** The resistance is  $8.00 \ \Omega$ .

**Strategy**

Use Ohm's law, the current, and the resistance of the second load to obtain the potential drop across it.

Add the potential drops across each resistor to obtain the potential difference of the battery.

**(b)** The potential difference of the battery is 224 V.

**Strategy**

Use the equation for resistance of a series circuit.

**(c)** The equivalent resistance is 32.0  $\Omega$ .

**Validate**

Using the equivalent resistance in part (c) and the current gives a check for the potential difference in part (b).

$$V_s = I_s + R_s = (7.00 \text{ A}) + (32.0 \text{ } \Omega) = 224 \text{ V}$$

**Calculations**

$$\begin{aligned} V_2 &= I_2 R_2 \\ &= (7.00 \text{ A})(24.0 \text{ } \Omega) \\ &= 168 \text{ V} \end{aligned}$$

$$\begin{aligned} V_s &= V_2 + V_2 \\ &= 168 \text{ V} + 56 \text{ V} \\ &= 2.24 \times 10^2 \text{ V} \end{aligned}$$

**Calculations**

$$\begin{aligned} R_s &= R_1 + R_2 \\ &= 8.0 \text{ } \Omega + 24.0 \text{ } \Omega \\ &= 32.0 \text{ } \Omega \end{aligned}$$

**Solutions for Practice Problems****Student Textbook page 638****31. Frame the Problem**

- Since all the resistors are in series, the formula for the equivalent resistance for a series circuit applies to the problem.
- Ohm's law applies to each individual circuit element.

**Identify the Goal**

The resistance of the third load,  $R_3$

**Variables and Constants**

Involved in the Problem		Known	Unknown
$R_1$	$V_1$	$I_s = 1.50 \text{ A}$	$V_1$
$R_2$	$V_2$	$R_1 = 42.0 \text{ } \Omega$	$V_3$
$R_3$	$V_3$	$V_3 = 111 \text{ V}$	$I_1$
$R_s$	$V_s$	$V_s = 240 \text{ } \Omega$	$I_2$
$I_1$			$I_3$
$I_2$			$R_2$
$I_3$			$R_3$
$I_s$			$R_s$

**Strategy**

Since the circuit has only one closed loop the current is the same everywhere in the circuit.

Use Ohm's law, the current, and the resistance of the first resistor to find the potential drop across it.

**Calculations**

$$I_1 = I_2 = I_3 = I_s = 1.50 \text{ A}$$

$$V_1 = I_1 R_1 = (1.5 \text{ A})(42.0 \text{ } \Omega) = 63.0 \text{ V}$$

Calculate the potential drop across the third resistor by subtracting the potential difference of the battery with the potential drop across the first two loads.

Apply Ohm's law to find the resistance of the third load.

$$\begin{aligned} V_3 &= V_S - V_1 - V_2 \\ &= 240 \text{ V} - 111 \text{ V} - 63.0 \text{ V} \\ &= 66.0 \text{ V} \end{aligned}$$

$$V_3 = I_3 R_3$$

Substitute first

$$\begin{aligned} 66.0 \text{ V} &= (1.50 \text{ A}) R_3 \\ 66.0 \text{ V} \cdot \frac{1}{1.50 \text{ A}} &= (1.50 \text{ A}) \frac{R_3}{1.50 \text{ A}} \\ R_3 &= \frac{66.0 \text{ V}}{1.50 \text{ A}} \\ R_3 &= 44.0 \Omega \end{aligned}$$

Solve for  $R_3$  first

$$\begin{aligned} V_3 &= I_3 R_3 \\ V_3 \cdot \frac{1}{I_3} &= I_3 \frac{R_3}{I_3} \\ R_3 &= \frac{66.0 \text{ V}}{1.50 \text{ A}} \\ R_3 &= 44.0 \Omega \end{aligned}$$

The resistance of the third load is  $44.0 \Omega$ .

### Validate

The units combine to give ohms, which is the correct unit for resistance.


$\frac{1}{R_S} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{6220.8}{69\,984 \Omega}$ , and inverting, you get  $R_S = 11.2 \Omega$ , as you should.

## Solutions for Practice Problems

### Student Textbook page 642
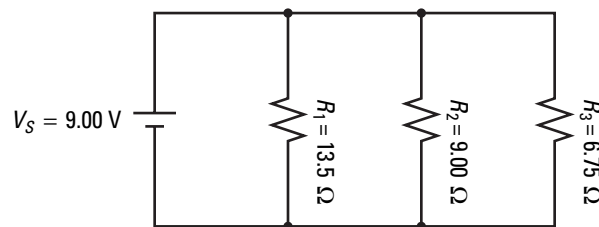
#### 32. Frame the Problem

- Since all the resistors are in parallel, the potential difference across each load is the same as the potential difference provided by the battery.
- The potential difference across the battery and the current entering and leaving the battery would be unchanged if the three loads would be replaced with one load having the equivalent resistance.
- After the current leaves the battery, it reaches branch points where it separates, and part of the current runs through each load.
- Ohm's law applies to each individual load and to the combined load.



### Identify the Goal

The current through each load  
The equivalent resistance

**Variables and Constants**

Involved in the Problem		Known	Unknown
$R_1$	$V_1$	$R_1 = 13.5 \Omega$	$V_1$
$R_2$	$V_2$	$R_2 = 9.00 \Omega$	$V_2$
$R_3$	$V_3$	$R_3 = 6.75 \Omega$	$V_3$
$R_S$	$V_S$	$V_S = 9.00 \text{ V}$	$R_S$
$I_1$			$I_1$
$I_2$			$I_2$
$I_3$			$I_3$
$I_S$			$I_S$

**Strategy**

Use Ohm's law, in terms of the current to find the current through the three loads. Use the fact that  $1 \frac{\text{V}}{\Omega}$  is equivalent to 1 A.

Use the equation for resistors in parallel and apply it to the three loads.

Substitute the values and add.

Find a common denominator. Add.

Invert both sides of the equation.

Divide

The currents are 0.667 A, 1.00 A and 1.33 A respectively. The equivalent resistance is  $3.00 \Omega$ .

**Calculations**

$$I_1 = \frac{9.00 \text{ V}}{13.5 \Omega} = 0.667 \text{ A}$$

$$I_2 = \frac{9.00 \text{ V}}{9.00 \Omega} = 1.00 \text{ A}$$

$$I_3 = \frac{9.00 \text{ V}}{6.75 \Omega} = 1.33 \text{ A}$$

$$\frac{1}{R_S} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_S} = \frac{1}{13.5 \Omega} + \frac{1}{9.00 \Omega} + \frac{1}{6.75 \Omega}$$

$$\begin{aligned} \frac{1}{R_S} &= \frac{60.75}{820.125 \Omega} + \frac{91.125}{820.125 \Omega} + \frac{121.5}{820.125 \Omega} \\ &= \frac{273.375}{820.125 \Omega} \end{aligned}$$

$$R_S = \frac{820.375 \Omega}{273.375}$$


$$R_S = 3.00 \Omega$$

**Validate**

If you add all the currents through each load ( $I_1 + I_2 + I_3 = I_S = 3.0 \text{ A}$ ) and multiply it by the equivalent resistance ( $R_S I_S = (3.0 \Omega)(3.0 \text{ A}) = 9.00 \text{ V}$ ) you get the applied voltage, as you should.

**33. Frame the Problem**

- Since all the resistors are in parallel, the potential difference across each load is the same as the potential difference provided by the battery.
- The potential difference across the battery and the current entering and leaving the battery would be unchanged if the two loads would be replaced with one load having the equivalent resistance.
- After the current leaves the battery, it reaches branch points where it separates, and part of the current runs through each load.
- Ohm's law applies to each individual load or to the combined load.

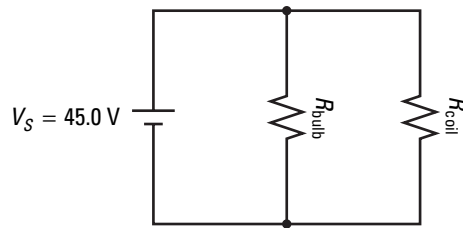**Identify the Goal**

The resistance of the light bulb,  $R_{\text{bulb}}$

The resistance of the coil,  $R_{\text{coil}}$

The equivalent resistance of the circuit,  $R_S$

**Variables and Constants****Involved in the Problem**

$$R_{\text{coil}} \quad R_{\text{bulb}}$$

$$I_{\text{bulb}}$$

$$I_{\text{coil}}$$

$$R_S$$

**Known**

$$I_S = 9.75 \text{ A}$$

$$I_{\text{coil}} = 7.50 \text{ A}$$

$$V_S = 45.0 \text{ V}$$

**Unknown**

$$R_S$$

$$I_{\text{bulb}}$$

$$R_{\text{bulb}}$$

$$R_{\text{coil}}$$

**Strategy**

Find the current through the bulb using the source current and the current through the coil.

Use Ohm's law, in term of the resistance, to solve resistance of the bulb and that of the coil.

Use the equation for resistors in parallel and apply it to the two loads.

Substitute the values and add.

Find a common denominator.  
Add.

Invert both sides of the equation.

Divide

The resistance of the coil is  $6.00 \Omega$  and that of the bulb is  $20.0 \Omega$ . The equivalent resistance is  $4.62 \Omega$ .

**Validate**

If you multiply the source current by the equivalent resistance ( $R_S I_S = (4.62 \Omega)(9.75 \text{ A}) = 45.0 \text{ V}$ ), you get the applied voltage.

**Calculations**

$$\begin{aligned} I_{\text{bulb}} &= I_S - I_{\text{coil}} \\ &= 9.75 \text{ A} - 7.50 \text{ A} \\ &= 2.25 \text{ A} \end{aligned}$$

$$R_{\text{bulb}} = \frac{45.0 \text{ V}}{2.25 \text{ A}} = 20.0 \Omega$$

$$R_{\text{coil}} = \frac{45.0 \text{ V}}{7.50 \text{ A}} = 6.00 \Omega$$

$$\frac{1}{R_S} = \frac{1}{R_{\text{bulb}}} + \frac{1}{R_{\text{coil}}}$$

$$\frac{1}{R_S} = \frac{1}{20.0 \Omega} + \frac{1}{6.00 \Omega}$$

$$\begin{aligned} \frac{1}{R_S} &= \frac{6.00}{120 \Omega} + \frac{20.0}{120 \Omega} \\ &= \frac{26.0}{120 \Omega} \end{aligned}$$

$$R_S = \frac{120 \Omega}{26.0}$$

$$R_S = 4.62 \Omega$$


**Solutions for Practice Problems**

Student Textbook page 642

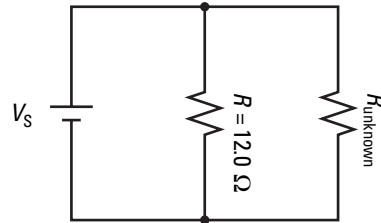**34. Frame the Problem**

- Since all the resistors are in parallel, the potential difference across each load is the same as the potential difference provided by the battery.

- The potential difference across the battery and the current entering and leaving the battery would be unchanged if the two loads would be replaced with one load having the equivalent resistance.
- After the current leaves the battery, it reaches branch points where it separates, and part of the current runs through each load.
- Ohm's law applies to each individual load or to the combined load.



**Identify the Goal**

The unknown resistance,  $R_{\text{unknown}}$   
 The equivalent resistance,  $R_S$

**Variables and Constants**

Involved in the Problem		Known	Unknown
$R_{\text{known}}$	$R_{\text{unknown}}$	$I_{\text{known}} = 3.20 \text{ A}$	$R_S$
$I_{\text{unknown}}$	$V_S$	$R_{\text{known}} = 12.0 \Omega$	$V_S$
$I_{\text{known}}$	$R_S$	$I_{\text{unknown}} = 4.80 \text{ A}$	$R_{\text{unknown}}$

**Strategy**

Find the applied voltage using Ohm's law with the resistance and the current of the applied voltage.

Use Ohm's law, in term of the resistance, to solve resistance of the unknown load.

Use the equation for resistors in parallel and apply it to the two loads.

Substitute the values and add.

Find a common denominator. Add.

Invert both sides of the equation.

Divide

The resistance of the unknown load is  $8.00 \Omega$ . The equivalent resistance is  $4.80 \Omega$ .

**Calculations**

$$V_S = I_{\text{known}} R_{\text{known}} = (3.20 \text{ A})(12.0 \Omega)$$

$$V_S = 38.4 \text{ V}$$

$$R_{\text{unknown}} = \frac{38.4 \text{ V}}{4.80 \text{ A}} = 8.00 \Omega$$

$$\frac{1}{R_S} = \frac{1}{R_{\text{unknown}}} + \frac{1}{R_{\text{known}}}$$

$$\frac{1}{R_S} = \frac{1}{8.00 \Omega} + \frac{1}{12.0 \Omega}$$

$$\begin{aligned} \frac{1}{R_S} &= \frac{12.0}{96.0 \Omega} + \frac{8.00}{96.0 \Omega} \\ &= \frac{20.0}{96.0 \Omega} \end{aligned}$$

$$R_S = \frac{96 \Omega}{20.0}$$

$$R_S = 4.80 \Omega$$

**Validate**


If you add all the currents through each load ( $I_S = I_{\text{known}} + I_{\text{unknown}} = 3.20 \text{ A} + 4.80 \text{ A} = 8.00 \text{ A}$ ) and multiply it by the equivalent resistance ( $R_S I_S = (4.80 \Omega)(8.00 \text{ A}) = 38.4 \text{ V}$ ) you get the applied voltage, as it should be.

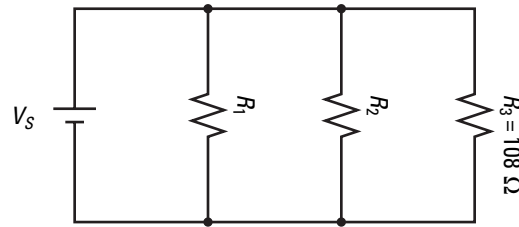**35. Frame the Problem**

- Since all the resistors are in parallel, the potential difference across each load is the same as the potential difference provided by the battery.
- The potential difference across the battery and the current entering and leaving the battery would be unchanged if the three loads would be replaced with one load having the equivalent resistance.



- After the current leaves the battery, it reaches branch points where it separates, and part of the current runs through each load.
- Ohm's law applies to each individual load or to the combined load.



### Identify the Goal

The currents through each load,  $I_1$ ,  $I_2$ , and  $I_3$

The equivalent resistance,  $R_S$

### Variables and Constants

Involved in the Problem		Known	Unknown
$R_1$	$I_1$	$I_1 = 2.50 \text{ A}$	$R_1$
$R_2$	$I_2$	$I_2 = 1.80 \text{ A}$	$R_2$
$R_3$	$I_3$	$R_3 = 108 \text{ } \Omega$	$R_S$
$R_S$	$I_S$	$I_S = 4.80 \text{ A}$	$I_3$
$V_S$			$V_S$

### Strategy

Calculate the current through the third load.

Use Ohm's law to find the voltage of the source using the resistance of the third load and the current through it.

Use Ohm's law, in term of the resistance, to solve resistance of the unknown load.

**(a)** The equivalent resistance is  $11.2 \text{ } \Omega$ .

Use Ohm's law, in term of the resistance, to solve resistance of the first and second load.

**(b)** The resistance of the first and second loads are  $21.6 \text{ } \Omega$  and  $30.0 \text{ } \Omega$  respectively.

### Validate

If you use the three resistances to calculate the equivalent resistance, you get  $\frac{1}{R_S} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{6220.8}{69984 \text{ } \Omega}$ , and inverting, you get  $R_S = 11.2 \text{ } \Omega$ , as you should.

### Calculations

$$\begin{aligned} I_3 &= I_S - I_1 - I_2 \\ &= 4.80 \text{ A} - 2.50 \text{ A} - 1.80 \text{ A} \\ &= 0.500 \text{ A} \end{aligned}$$

$$\begin{aligned} V_S &= I_3 R_3 \\ &= (0.500 \text{ A})(108 \text{ } \Omega) \\ &= 54.0 \text{ V} \end{aligned}$$

$$V_S = \frac{54.0 \text{ V}}{4.80 \text{ A}} = 11.2 \text{ } \Omega$$

$$R_1 = \frac{54.0 \text{ V}}{2.50 \text{ A}} = 21.6 \text{ } \Omega$$

$$R_2 = \frac{54.0 \text{ V}}{1.80 \text{ A}} = 30.0 \text{ } \Omega$$

## Solutions for Practice Problems

Student Textbook page 646

### 36. Frame the Problem

- The circuit consists of a battery and four loads. The battery generates a specific potential difference across the poles.

- The current driven by the potential difference of the battery depends on the effective resistance of the entire circuit.
- The circuit has three groups of resistors. Resistors  $R_1$  and  $R_2$  are in series with each other. Resistors  $R_3$  and  $R_4$  are in series with each other. Finally, the  $R_1$ – $R_2$  group is in parallel with the  $R_3$ – $R_4$  group.
- Define the  $R_1$ – $R_2$  group as Group A and the  $R_3$ – $R_4$  group as Group B. Sketch the circuit with equivalent loads,  $R_A$  and  $R_B$ .
- Now, define the parallel group consisting of  $R_A$  and  $R_B$  as Group C. Sketch the circuit with the equivalent load,  $R_C$ .
- Load  $R_C$  is the equivalent resistance of the entire circuit.
- The potentials across groups A and B are the same.
- The current through  $R_1$  and  $R_2$  is the same.

### Identify the Goal


The equivalent resistance,  $R_C$

The current through  $R_1$

The potential difference across  $R_3$

### Variables and Constants

Involved in the Problem		Known	Unknown
$R_1$	$I_1$	$R_1 = 26.0 \Omega$	$R_A$
$R_2$	$I_2$	$R_2 = 38.0 \Omega$	$R_B$
$R_3$	$I_3$	$R_3 = 61.0 \Omega$	$R_C$
$R_4$	$I_4$	$R_4 = 35.0 \Omega$	$V_3$
$R_A$	$I_S$	$V_S = 144 \text{ V}$	$I_1$
$R_B$	$I_A$		$I_2$
$R_C$	$I_B$		$I_3$
$V_3$			$I_4$
$V_S$			$I_A$
			$I_B$

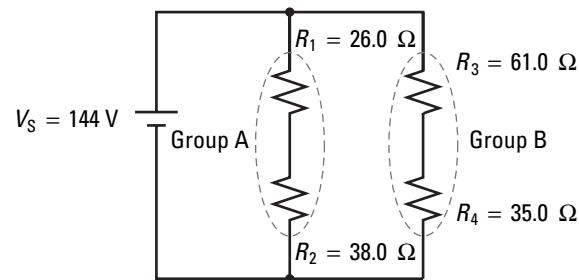

### Strategy

Find the equivalent resistance for the series Group A resistors.

Find the equivalent resistance for the series Group B resistors.

Use the equation for resistors in parallel and apply it to the two groups A and B.

Substitute the values and add.

### Calculations

$$\begin{aligned} R_A &= R_1 + R_2 \\ &= 26.0 \Omega + 38.0 \Omega \\ &= 64.0 \Omega \end{aligned}$$

$$\begin{aligned} R_B &= R_3 + R_4 \\ &= 61.0 \Omega + 35.0 \Omega \\ &= 96.0 \Omega \end{aligned}$$

$$\frac{1}{R_C} = \frac{1}{R_A} + \frac{1}{R_B}$$

$$\frac{1}{R_C} = \frac{1}{64.0 \Omega} + \frac{1}{96.0 \Omega}$$

Find a common denominator. Add.

$$\begin{aligned}\frac{1}{R_C} &= \frac{96.0}{6144 \Omega} + \frac{64.0}{6144 \Omega} \\ &= \frac{160}{6144 \Omega}\end{aligned}$$

Invert both sides of the equation.

$$R_C = \frac{6144 \Omega}{160}$$

Divide.

$$R_C = 38.4 \Omega$$

(a) The equivalent resistance is  $38.4 \Omega$ .

### Strategy

Use Ohm's law, in terms of current to find the current in group A and group B.

### Calculations

$$I_A = \frac{V_S}{R_A} = \frac{144 \text{ V}}{64.0 \Omega} = 2.25 \text{ A} = I_1 = I_2$$

$$I_B = \frac{V_S}{R_B} = \frac{144 \text{ V}}{96.0 \Omega} = 1.50 \text{ A} = I_3 = I_4$$

(b) The current through resistance  $R_1$  is  $2.25 \text{ A}$ .

### Strategy

Use Ohm's law to find the voltage of  $R_3$  using the resistance of the third load and the current through it.

### Calculations

$$\begin{aligned}V_3 &= I_3 R_3 \\ &= (1.50 \text{ A})(61.0 \Omega) \\ &= 91.5 \text{ V}\end{aligned}$$

(c) The potential difference across  $R_3$  is  $91.5 \text{ V}$ .

### Validate

If you add all the currents through each group ( $I_S = I_B + I_A = 2.25 \text{ A} + 1.50 \text{ A} = 3.75 \text{ A}$ ) and multiply it by the equivalent resistance ( $R_C I_S = (38.4 \Omega)(3.75 \text{ A}) = 144 \text{ V}$ ) you get the applied voltage.

## Solutions for Practice Problems

### Student Textbook page 646

#### 37. Frame the Problem

- The circuit consists of a battery and three loads. The battery generates a specific potential difference across the poles.
- The current driven by the potential difference of the battery depends on the effective resistance of the entire circuit.
- The circuit has two groups of resistors. Resistors  $R_1$  and  $R_2$  are in parallel with each other. Load  $R_3$  is in series with the  $R_1$ - $R_2$  group.
- Define the  $R_1$ - $R_2$  group as Group A and sketch the circuit with equivalent load,  $R_A$ .
- Now, define the parallel group consisting of  $R_A$  and  $R_1$  as Group B. Sketch the circuit with the equivalent load,  $R_B$ .
- Load  $R_B$  is the equivalent resistance of the entire circuit.
- The potential across  $R_1$  and  $R_2$  are the same.

#### Identify the Goal

The equivalent resistance,  $R_B$


The potential difference across  $R_3$

The current through  $R_1$

#### Variables and Constants

Involved in the Problem		Known	Unknown
$V_1$	$I_1$	$R_1 = 15.0 \Omega$	$I_1$
$V_2$	$I_2$	$R_2 = 25.0 \Omega$	$I_2$
$V_3$	$I_3$	$R_3 = 6.00 \Omega$	$I_3$
$V_S$	$I_S$	$V_S = 25.0 \text{ V}$	$I_S$

- |       |       |
|-------|-------|
| $R_1$ | $R_A$ |
| $R_2$ | $R_B$ |
| $R_3$ | $V_1$ |
| $R_A$ | $V_2$ |
| $R_B$ | $V_3$ |

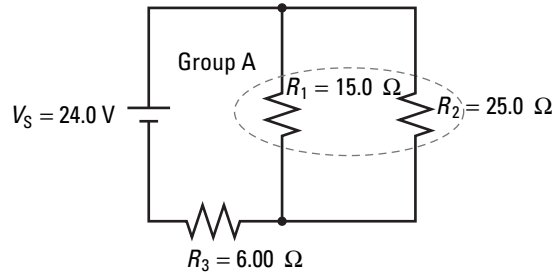

**Strategy**

Find the equivalent resistance for the series Group A resistors.

Find the equivalent resistance for the series Group B resistors.

Use the equation for resistors in parallel and apply it to find the equivalent resistance of the group A of resistors.

Substitute the values and add.

Find a common denominator. Add.

Invert both sides of the equation.

Divide

Add the resistance of group A with the third load, which are in series.

**(a)** The equivalent resistance is  $15.4 \Omega$ .

**Strategy**

Use Ohm's law, in terms of current to find the source current.

Use Ohm's law to find the voltage of  $R_3$  using the resistance of the third load and the current through it.

**(b)** The potential difference across  $R_3$  is  $9.76 \text{ V}$ .

**Strategy**

Subtract the potential drop due to  $R_3$  from the source voltage to obtain the potential drop across the parallel resistors.

Use Ohm's law, in terms of current to find the current through  $R_1$ .

**(c)** The current through resistance  $R_1$  is  $1.02 \text{ A}$ .

**Calculations**

$$\begin{aligned} R_A &= R_1 + R_2 \\ &= 26.0 \Omega + 38.0 \Omega \\ &= 64.0 \Omega \end{aligned}$$

$$\begin{aligned} R_B &= R_3 + R_4 \\ &= 61.0 \Omega + 35.0 \Omega \\ &= 96.0 \Omega \end{aligned}$$

$$\frac{1}{R_A} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_A} = \frac{1}{15.0 \Omega} + \frac{1}{25.0 \Omega}$$

$$\frac{1}{R_A} = \frac{25.0}{375 \Omega} + \frac{15.0}{375 \Omega} = \frac{40}{375 \Omega}$$

$$R_A = \frac{375 \Omega}{40}$$

$$R_A = 9.37 \Omega$$

$$\begin{aligned} R_B &= 9.37 \Omega + 6.00 \Omega \\ &= 15.4 \Omega \end{aligned}$$

**Calculations**

$$I_S = \frac{V_S}{R_B} = \frac{25.0 \text{ V}}{15.4 \Omega} = 1.63 \text{ A}$$

$$\begin{aligned} V_3 &= I_S R_3 \\ &= (1.63 \text{ A})(6.00 \Omega) \\ &= 9.76 \text{ V} \end{aligned}$$

**Calculations**

$$\begin{aligned} V_1 &= V_2 = V_S - V_3 \\ &= 25.0 \text{ V} - 9.76 \text{ V} \\ &= 15.2 \text{ V} \end{aligned}$$

$$I_S = \frac{V_S}{R_B} = \frac{25.0 \text{ V}}{15.4 \Omega} = 1.63 \text{ A}$$

**Validate**

The equivalent resistance came out in amperes, the potential difference in volts and the equivalent resistance in ohms, which are all the correct units.

**Solutions for Practice Problems**

Student Textbook page 649

**38. (a) Frame the Problem**

- The battery has an internal resistance with an *emf* in a closed circuit.
- There is a current through the circuit so the terminal voltage will not be the *emf*.
- Therefore terminal voltage will be less than that of the *emf*.

**Identify the Goal**

The terminal voltage ( $V_S$ ) of the battery

**Variables and Constants**

Involvement in the Problem	Known	Unknown
$E$	$E = 15.0 \text{ V}$	$V_{\text{int}}$
$V_{\text{int}}$	$r = 0.0800 \ \Omega$	$V_S$
$V_S$	$I_S = 2.50 \text{ A}$	
$I_S$		
$r$		

**Strategy**

Use Ohm's law to find the internal potential drop across the battery using the internal resistance of the battery and the current through it.

Multiply.

$1 \text{ A} \cdot \Omega$  is equivalent to 1 V, thus

Use this potential difference to find the Terminal voltage.

Subtract.

The terminal voltage is 14.8 V when the current is 2.50 A.

**Calculations**

$$V_{\text{int}} = I_S r$$

$$V_{\text{int}} = (2.50 \text{ A})(0.0800 \ \Omega)$$

$$V_{\text{int}} = 0.20 \text{ V}$$

$$V_S = E - V_{\text{int}}$$

$$V_S = 15.0 \text{ V} - 0.20 \text{ V}$$

**Validate**

Since the potential difference loss due to the battery is small compared to the terminal voltage, the result is reasonable (just over 1% of terminal voltage).

**(b) Frame the Problem**

- The battery has an internal resistance with an *emf* in a closed circuit.
- There is a bigger current through the circuit than in part (a) so the terminal voltage will be smaller than in part (a).

**Identify the Goal**

The terminal voltage ( $V_S$ ) of the battery

**Variables and Constants**

Involvement in the Problem	Known	Unknown
$E$	$E = 15.0 \text{ V}$	$V_{\text{int}}$
$V_{\text{int}}$	$r = 0.0800 \ \Omega$	$V_S$

$$V_S = 15.0 \text{ V}$$

$$I_S = 2.50 \text{ A}$$

$$r = 0.0800 \text{ } \Omega$$

**Strategy**

Use Ohm's law to find the internal potential drop across the battery using the internal resistance of the battery and the current through it.

Multiply.

1 A· $\Omega$  is equivalent to 1 V, thus

Use this potential difference to find the Terminal voltage.

Subtract.

The terminal voltage is 14.6 V when the current is 5.00 A.

**Calculations**

$$V_{\text{int}} = I_S r$$

$$V_{\text{int}} = (5.00 \text{ A})(0.0800 \text{ } \Omega)$$

$$V_{\text{int}} = 0.40 \text{ V}$$

$$V_S = E - V_{\text{int}}$$

$$V_S = 15.0 \text{ V} - 0.40 \text{ V}$$

$$V_S = 14.6 \text{ V}$$

**Validate**

As expected, the potential difference loss due to the battery is larger than in part (a). However, it is still much smaller than the terminal voltage, just less than 3% of it.

**39. (a) Frame the Problem**

- The battery has an internal resistance with an *emf* in a closed circuit.
- There is a current through the circuit so the *emf* will be greater than the terminal voltage.
- The *emf* will depend directly on the current flowing through the circuit.

**Identify the Goal**

The *emf* of the battery,  $E$

**Variables and Constants****Involved in the Problem**

$E$

$V_{\text{int}}$

$V_S$

$I_S$

$r$

**Known**

$$V_S = 10.6 \text{ V}$$

$$r = 0.120 \text{ } \Omega$$

$$I_S = 7.00 \text{ A}$$

**Unknown**

$V_{\text{int}}$

$E$

**Strategy**

Use Ohm's law to find the internal potential drop across the battery using the internal resistance of the battery and the current through it.

Multiply.

1 A· $\Omega$  is equivalent to 1 V, thus

Use this potential difference to find the terminal voltage.

Add.

Round up.

The *emf* is 11.4 V when the potential drop across the battery is 0.84 V.

**Calculations**

$$V_{\text{int}} = I_S r$$

$$V_{\text{int}} = (7.00 \text{ A})(0.120 \text{ } \Omega)$$

$$V_{\text{int}} = 0.84 \text{ V}$$

$$E = V_{\text{int}} + V_S$$

$$E = 10.6 \text{ V} + 0.84 \text{ V}$$

$$E = 11.4 \text{ V}$$

**Validate**

The *emf* of the battery is larger than the terminal voltage as it should be. Also, the potential difference loss due to the battery's internal resistance is small just over 7 percent of the *emf*.

**(b) Frame the Problem**

- The battery has an internal resistance with an *emf* in a closed circuit.
- There is a current through the circuit so the terminal voltage will be smaller than the *emf*.
- The terminal voltage will depend directly on the current flowing through the circuit.

**Identify the Goal**

The terminal voltage ( $V_S$ ) of the battery from the *emf* solved for in part (a).

**Variables and Constants**

Involved in the Problem	Known	Unknown
$E$	$V_S = 11.4 \text{ V}$	$V_{\text{int}}$
$V_{\text{int}}$	$r = 0.120 \ \Omega$	$E$
$V_S$	$I_S = 2.20 \text{ A}$	
$I_S$		
$r$		

**Strategy**

Use Ohm's law to find the internal potential drop across the battery using the internal resistance of the battery and the current through it.

Multiply.

$1 \text{ A} \cdot \Omega$  is equivalent to 1 V, thus

Use this potential difference to find the terminal voltage.

Subtract.

Round up.

The terminal voltage is 11.2 V when the potential drop across the battery is 0.26 V.

**Calculations**

$$V_{\text{int}} = I_S r$$

$$V_{\text{int}} = (2.20 \text{ A})(0.120 \ \Omega)$$

$$V_{\text{int}} = 0.26 \text{ V}$$

$$V_S = E - V_{\text{int}}$$

$$V_S = 11.44 \text{ V} - 0.26 \text{ V}$$

$$V_S = 11.2 \text{ V}$$

**Validate**

The terminal voltage is smaller than the *emf* as it should be. Also, the potential difference loss due to the battery's internal resistance is small just over 2 % of the *emf*.

**Solutions for Practice Problems****Student Textbook page 655****40. Frame the Problem**

- The power in this case is the rate at which the electric energy is converted to heat when using the toaster.
- You can calculate the current from the power rating of the toaster and from its potential difference.
- The resistance of the toaster will be related to the potential difference and to the current drawn by the toaster.

**Identify the Goal**

- (a) The current drawn from the toaster
- (b) The resistance of the toaster

**Variables and Constants**

Involved in the Problem	Known	Unknown
$P$	$P = 875 \text{ W}$	$I$
$I$	$V = 120 \text{ V}$	$R$
$V$		
$R$		

**Strategy**

Use the relation between the power, current and potential energy.

Solve for the current.

Divide.

$1 \frac{\text{W}}{\text{V}}$  is equivalent to 1 A.

Round up.

- (a) The current that the toaster draws is 7.3 A.

**Calculations**

$$P = IV$$

$$\frac{P}{V} = \frac{I}{1}$$

$$I = \frac{875 \text{ W}}{120 \text{ V}}$$

$$I = 7.29 \text{ A}$$

$$I = 7.3 \text{ A}$$

**Strategy**

Use Ohm's law, which relates the potential difference to the current and the resistance.

Solve for the resistance.

Divide.

$1 \frac{\text{V}}{\text{A}}$  is equivalent to  $\Omega$ .

Round down.

The resistance of the toaster is 16  $\Omega$ .

**Calculations**

$$V = IR$$

$$\frac{V}{I} = \frac{R}{1}$$

$$R = \frac{120 \text{ V}}{7.3 \text{ A}}$$

$$R = 16.4 \Omega$$

$$R = 16 \Omega$$

**Validate**

The units give amperes, which is the correct unit of current.

Power over potential difference is current since  $\frac{P}{V} = \frac{\frac{\text{A}\cdot\text{V}\cdot\text{s}}{\text{s}}}{\frac{\text{A}\cdot\text{V}\cdot\text{s}}{\text{s}}}$  and this is the definition of current. For part (b), the units give ohms, which is the correct unit of resistance.

**41. (a) Frame the Problem**

- The light bulb has a resistance so when there is a potential difference there is a current.
- The power output of the light bulb will be related to the current and the voltage applied.

**Identify the Goal**

The power output of the light bulb

**Variables and Constants**

Involved in the Problem	Known	Unknown
$R$	$R = 240 \Omega$	$P$
$I$	$V = 120 \text{ V}$	$I$
$P$		$V$
$V$		



**Strategy**

Use Ohm's law that relates the potential difference to the current and the resistance.

Solve for the current.

Use the relation between the power, current and potential energy.

Substitute  $I$  with its expression in terms of  $V$  and  $R$  into the equation of the power.

Simplify.

Divide.

$1 \frac{V^2}{\Omega}$  is equivalent to 1 W.

The power output of the bulb is 60 W.

**Calculations**

$$V = IR$$

$$\frac{V}{R} = \frac{I}{\frac{R}{R}}$$

$$P = IV$$

$$P = \frac{V}{R} V$$

$$P = \frac{V^2}{R}$$

$$P = \frac{(120 \text{ V})^2}{240 \Omega}$$

$$P = 60 \text{ W}$$

**Validate**

The units give watts, which is the correct unit of power.

**(b) Frame the Problem**

- The light bulb has a resistance so when there is a potential difference there is a current.
- The power output of the light bulb will be related to the current and the voltage applied but it will be less than part (a) since there is less voltage applied to the bulb.

**Identify the Goal**

The power output of the light bulb

**Variables and Constants****Involved in the Problem**

$R$

$I$

$P$

$V$

**Known**

$$P = 7.3 \text{ A}$$

$$V = 80.0 \text{ V}$$

**Unknown**

$I$

$P$

**Strategy**

Use Ohm's law, which relates the potential difference to the current and the resistance.

Solve for the current.

Use the relation between the power, current and potential energy.

Substitute  $I$  with its expression in terms of  $V$  and  $R$  into the equation of the power.

Simplify.

Divide.

$1 \frac{V^2}{\Omega}$  is equivalent to 1 W.

The power output of the bulb is 27 W.

**Calculations**

$$V = IR$$

$$\frac{V}{R} = \frac{I}{\frac{R}{R}}$$

$$P = IV$$

$$P = \frac{V}{R} V$$

$$P = \frac{V^2}{R}$$

$$P = \frac{80.0 \text{ V}^2}{240 \Omega}$$

$$P = 27 \text{ W}$$

**Validate**

The units give watts, which is the correct unit of power.

**(c) Frame the Problem**

- The light bulb has a resistance so when there is a potential difference there is a current.
- The resistance of the bulb should be decreased to get the same power output as in part (a) (power is proportional to the inverse of resistance).

**Identify the Goal**

The resistance needed to get the same power output as in part (a) with the voltage in part (b)

**Variables and Constants**

Involved in the Problem	Known	Unknown
$R$	$P = 60 \text{ W}$	$I$
$I$	$V = 80.0 \text{ V}$	$R$
$P$		
$V$		

**Strategy**

Use Ohm's law, which relates the potential difference to the current and the resistance.

Solve for the current.

Use the relation between the power, current and potential energy.

Substitute  $I$  with its expression in terms of  $V$  and  $R$  into the equation of the power.

Simplify.

Solve for  $R$ .

Divide.

$1 \frac{\text{V}^2}{\text{W}}$  is equivalent to  $1 \Omega$ .

The required resistance of the bulb is  $1.1 \times 10^2 \Omega$ .

**Calculations**

$$V = IR$$

$$\frac{V}{R} = \frac{R \cdot I}{R}$$

$$P = IV$$

$$P = \frac{V}{R} V$$

$$P = \frac{V^2}{R}$$

$$P \frac{R}{P} = \frac{R}{P} \frac{V^2}{R}$$

$$R = \frac{(80.0 \text{ V})^2}{60 \text{ W}}$$

$$R = 1.1 \times 10^2 \Omega$$

**Validate**

The units give ohms, which is the correct unit of resistance.

**42. (a) Frame the Problem**

- The power in this case is the rate at which the electric energy is converted to heat when using the heater.
- You can calculate the power from the resistance and the current of the heater.

**Identify the Goal**

The power output of the heater

**Variables and Constants**

Involved in the Problem	Known	Unknown
$P$	$R = 15 \Omega$	$V$
$I$	$I = 7.5 \text{ A}$	$P$
$R$		
$V$		

**Strategy**

Use the relation between the power, current and potential energy.

Use Ohm's law.

Substitute  $V$  from Ohm's law in the expression for the power.

Multiply.

$1 \Omega \cdot \text{A}^2$  is equivalent to  $1 \text{ W}$ .

Round down.

The power output of the heater is  $840 \text{ W}$ .

**Calculations**

$$P = IV$$

$$V = IR$$

$$P = I(IR)$$

$$P = RI^2$$

$$P = (15 \Omega)((7.5 \text{ A})^2)$$

$$P = 844 \text{ W}$$

$$P = 840 \text{ W}$$

**Validate**

The units give watts, which is the correct unit of power.

**(b) Frame the Problem**

- The power in this case is the rate at which the electric energy is converted to heat when using the heater.
- You can calculate the new current from part (a) and thus power from the resistance and the new current of the heater.

**Identify the Goal**

The power output of the heater

**Variables and Constants**

Involved in the Problem	Known	Unknown
$P$	$R = 15 \Omega$	$V$
$I$		$P$
$R$		$I$
$V$		

**Strategy**

Use the value of the current in part (a) and divide it by two to get the new current.

Divide.

Use the relation between the power, current and potential energy.

Use Ohm's law.

Substitute  $V$  from Ohm's law in the expression for the power.

Multiply.

$1 \Omega \cdot \text{A}^2$  is equivalent to  $1 \text{ W}$ .

The power output of the heater is one quarter of its original value in part (a), or  $211 \text{ W}$ .

**Calculations**

$$I = \frac{7.5 \text{ A}}{2}$$

$$I = 3.75 \text{ A}$$

$$P = IV$$

$$V = IR$$

$$P = I(IR)$$

$$P = RI^2$$

$$P = (15 \Omega)((3.25 \text{ A})^2)$$

$$P = 211 \text{ W}$$

**Validate**

The units give watts, which is the correct unit of power.

## Solutions for Practice Problems

Student Textbook page 658

### 43. Frame the Problem

- The power is the rate at which the electric energy is converted to another form of energy.
- You can calculate the power from the resistance and from the setting of the power supply.
- You can calculate the power outputs ratio and the potential differences ratio from the values found or given in part (a).

### Identify the Goal

- (a) The power output for two different power supplies
- (b) The power outputs ratio, the potential differences ratio, and the relationship between the two ratios

### Variables and Constants

Involved in the Problem	Known	Unknown
$P_a$	$R = 45 \Omega$	$P_a$
$P_b$	$V_a = 180 \text{ V}$	$P_b$
$V_a$	$V_b = 270 \text{ V}$	$I_a$
$V_b$		$I_b$
$R$		$P_a/P_b$
$I_a$		$V_a/V_b$
$I_b$		
$P_a/P_b$		
$V_a/V_b$		

### Strategy

Use Ohm's law that relates the potential difference to the current and the resistance for the supply.

Solve for the current.

Use the relation between the power, current and potential energy.

Substitute  $I_a$  with its expression in terms of  $V_a$  and  $R$  into the equation of the power.

Simplify.

Divide.

$1 \frac{V^2}{\Omega}$  is equivalent to 1 W.

Use the corresponding expression for power source b in terms of the potential difference and the resistance.

Divide.

$1 \frac{V^2}{\Omega}$  is equivalent to 1 W.

Round down.

- (a) Power source a outputs 720 W and power source b outputs  $1.6 \times 10^3$  W.

### Calculations

$$V_a = I_a R$$

$$\frac{V_a}{R} = \frac{I_a R}{R}$$

$$P_a = I_a V$$

$$P_a = \frac{V_a}{R} V_a$$

$$P_a = \frac{V_a^2}{R}$$

$$P_a = \frac{(180 \text{ V})^2}{45 \Omega}$$

$$P_a = 720 \text{ W}$$

$$P_b = \frac{V_b^2}{R}$$

$$P_b = \frac{(270 \text{ V})^2}{45 \Omega}$$

$$P_b = 1.62 \times 10^3 \text{ W}$$

$$P_b = 1.6 \times 10^3 \text{ W}$$

**Strategy**

Use the values for the power output calculated in part (a) for both power supplies and find their ratios.

Factorize the numerator and the denominator.

Simplify.

Use the values for the potential difference given in part (a) for both power supplies and find their ratios.

Factorize the numerator and the denominator.

Simplify.

Use the relation relating power, voltage and resistance for power supply a derived in (a).

Use the corresponding expression for power source b.

Take the ratio of these last two expressions.

Simplify.

**(b)** The ratio of the powers output is 4/9 and the ratio of the potential differences is 2/3. The relationship relating the two ratios is  $\frac{P_a}{P_b} = \left(\frac{V_a}{V_b}\right)^2$ .

**Calculations**

$$\frac{P_a}{P_b} = \frac{720 \text{ W}}{1.62 \times 10^3 \text{ W}}$$

$$\frac{P_a}{P_b} = \frac{(180)(4 \text{ W})}{(180)(9 \text{ W})}$$

$$\frac{P_a}{P_b} = \frac{4}{9}$$

$$\frac{V_a}{V_b} = \frac{180 \text{ V}}{270 \text{ V}}$$

$$\frac{V_a}{V_b} = \frac{(90)(2 \text{ V})}{(90)(3 \text{ V})}$$

$$\frac{V_a}{V_b} = \frac{2}{3}$$

$$P_a = \frac{V_a^2}{R}$$

$$P_b = \frac{V_b^2}{R}$$

$$\frac{P_a}{P_b} = \frac{\frac{V_a^2}{R}}{\frac{V_b^2}{R}}$$

$$\frac{P_a}{P_b} = \left(\frac{V_a}{V_b}\right)^2$$

**Validate**

The power outputs are in watts, which is correct. The ratios are dimensionless which is correct.

Using the fact that  $\frac{V_a}{V_b} = \frac{2}{3}$ , and using the relationship between the ratios, we find that  $\frac{P_a}{P_b} = \left(\frac{2}{3}\right)^2 = \frac{4}{9}$ , which confirms the formula relating the two ratios.

**44. Frame the Problem**

- The load has a resistance.
- The resistance will remain approximately the same even when a different current passes through it. Therefore, according to Ohm's law, the potential difference will be different.
- If both the current and the potential difference have changed, the power will probably be different.

**Identify the Goal**

The new power output

**Variables and Constants**

Involved in the Problem

$$P_6$$

$$P_{15}$$

$$V_6$$

$$V_{15}$$

$$R$$

Known

$$P_6 = 160 \text{ W}$$

$$I_6 = 6 \text{ A}$$

$$I_{15} = 15 \text{ A}$$

Unknown

$$P_{15}$$

$$R$$

$$V_6$$

$$V_{15}$$

$$I_6$$

$$I_{15}$$

**Strategy**

Find the voltage at 6 A.

Find the resistance.

Find the voltage at 15 A.

Find the power output at 15 A.

The power output is  $1.0 \times 10^3$  W.

**Validate**

The power is in a watt, which is correct, and it increases which is to be expected. In fact, the ratio of the power outputs is equal to the square of the ratio of the currents, as in problem 43.

**45. (a) Frame the Problem**

- The power is the rate at which the electric energy is converted to another form of energy from the circuit.
- You can calculate the power from the resistance and from the setting of the power supply by using Ohm's law as an intermediate step.

**Identify the Goal**

The power output

**Variables and Constants**

Involved in the Problem

$$P$$

$$V$$

$$I$$

$$R$$

Known

$$R = 25 \Omega$$

$$V = 100 \text{ V}$$

Unknown

$$I$$

$$P$$

**Strategy**

Find the current using Ohm's law.

Find the Power.

**Calculations**

$$P_6 = I_6 V_6$$

$$V_6 = \frac{P_6}{I_6}$$

$$V_6 = \frac{160 \text{ W}}{6.0 \text{ A}}$$

$$V_6 = 26.7 \text{ V}$$

$$R = \frac{V_6}{I_6}$$

$$R = \frac{26.7 \text{ V}}{6.0 \text{ A}}$$

$$R = 4.44 \Omega$$

$$V_{15} = I_{15} R$$

$$V_{15} = (15 \text{ A})(4.44 \Omega)$$

$$V_{15} = 66.7 \text{ V}$$

$$P_{15} = I_{15} V_{15}$$

$$P_{15} = (15 \text{ A})(66.7 \text{ V})$$

$$P_{15} = 1.0 \times 10^3 \text{ W}$$

**Calculations**

$$V = RI$$

$$I = \frac{V}{R}$$

$$I = \frac{100 \text{ V}}{25 \Omega}$$

$$I = 4 \text{ A}$$

$$P = VI$$

$$P = (100 \text{ V})(4 \text{ A})$$

$$P = 400 \text{ W}$$

The power output of the circuit is 400 W.

### Validate

The power has units of watts, which is correct.

### (b) Frame the Problem

- The power is the rate at which the electric energy is converted to another form of energy from the circuit.
- You can calculate the power from the equivalent resistance and from the setting of the power supply by using Ohm's law as an intermediate step.

### Identify the Goal

The power output

### Variables and Constants

Involvement in the Problem	Known	Unknown
$P$	$R_1 = 25 \Omega$	$I$
$V$	$R_2 = 25 \Omega$	$P$
$I$	$V = 100 \text{ V}$	$R_{\text{eq}}$
$R_2$		
$R_1$		
$R_{\text{eq}}$		

### Strategy

Find the equivalent resistance when  $R_1$  and  $R_2$  are connected in series.

Find the current using Ohm's law and the equivalent resistance.

Find the Power.

### Calculations

$$R_{\text{eq}} = R_1 + R_2$$

$$R_{\text{eq}} = 25 \Omega + 25 \Omega$$

$$R_{\text{eq}} = 50 \Omega$$

$$V = R_{\text{eq}} I$$

$$I = \frac{V}{R_{\text{eq}}}$$

$$I = \frac{100 \text{ V}}{50 \Omega}$$

$$I = 2 \text{ A}$$

$$P = VI$$

$$P = (100 \text{ V})(2 \text{ A})$$

$$P = 200 \text{ W}$$

The power is 200 W. Since the voltage is fixed and the resistance is increased, then (by Ohm's law) the current must decrease. Thus, the power must decrease.

### Validate

The power comes out in watts, which is the correct unit.

## Solutions for Practice Problems

### Student Textbook page 662

#### 46. Frame the Problem

- A light bulb will use energy at a rate of 192 W if it has a resistance of 12.0  $\Omega$ .
- Power, potential difference, and resistance are all related.

### Identify the Goal

The potential difference at which the light bulb is designed to operate

**Variables and Constants****Involved in the Problem** $R$  $P$  $V$ **Known**

$R = 12.0 \Omega$

$P = 192 \text{ W}$

**Unknown** $V$ **Strategy**

Use the relationship between power, potential difference and resistance.

**Calculations**

$$P = \frac{V^2}{R}$$

Solve for  $V$  first

$$PR = \frac{(V)^2}{R} R$$

$$PR = V^2$$

$$\sqrt{PR} = \sqrt{V^2}$$

$$V = \sqrt{(192 \text{ W})(12.0 \Omega)}$$

$$V = 48.0\sqrt{\text{W} \Omega}$$

$$V = 48.0 \text{ V}$$

Substitute first

$$192 \text{ W} = \frac{V^2}{12.0 \Omega}$$

$$(192 \text{ W})(12.0 \Omega)$$

$$= \frac{V^2}{12.0 \Omega} (12.0 \Omega)$$

$$V^2 = (192 \text{ W})(12.0 \Omega)$$

$$\sqrt{V^2} = \sqrt{(192 \text{ W})(12.0 \Omega)}$$

$$V = \sqrt{(192 \text{ W})(12.0 \Omega)}$$

$$V = 48.0\sqrt{\text{W} \Omega}$$

$$V = 48.0 \text{ V}$$

The potential difference is 48.0 V.

**Validate**

$$\text{Unit Check: } \sqrt{\text{W} \Omega} = \sqrt{\frac{\text{VC}}{\text{s}} \frac{\text{V}}{\text{A}}} = \sqrt{\frac{\text{V} \cancel{\text{C}} \text{V}}{\cancel{\text{s}} \cancel{\text{C}} \cancel{\text{A}}}} = \sqrt{\text{V}^2} = \text{V}$$

The units give volts, which is the correct unit of potential difference.

**47. Frame the Problem**

- The electric kettle will use energy at a rate of 960 W if connected to a 120 V line.
- Power, potential difference, and resistance are all related.

**Identify the Goal**

The resistance of the kettle

**Variables and Constants****Involved in the Problem** $R$  $P$  $V$ **Known**

$V = 120 \text{ V}$

$P = 160 \text{ W}$

**Unknown** $R$ **Strategy**

Use the relationship between power, potential difference and resistance.

**Calculations**

$$P = \frac{V^2}{R}$$

Solve for  $R$  first

$$PR = \frac{(V)^2}{R} R$$

$$PR = V^2$$

$$\frac{PR}{P} = \frac{V^2}{P}$$

$$R = \frac{V^2}{P}$$

Substitute first

$$960 \text{ W} = \frac{(120 \text{ V})^2}{R}$$

$$(960 \text{ W})R = \frac{(120 \text{ V})^2}{R} R$$

$$\frac{(960 \text{ W})R}{960 \text{ W}} = \frac{(120 \text{ V})^2}{960 \text{ W}}$$



$$R = \frac{(120 \text{ V})^2}{960 \text{ W}} \qquad R = \frac{(120 \text{ V})^2}{960 \text{ W}}$$

$$R = 15 \frac{\text{V}^2}{\text{W}} \qquad R = 15 \frac{\text{V}^2}{\text{W}}$$

$$R = 15 \Omega \qquad R = 15 \Omega$$

The resistance is  $15 \Omega$ .

### Validate

Unit Check:  $\frac{\text{V}^2}{\text{W}} = \frac{\text{J}^2/\text{C}^2}{\text{J/s}} = \left(\frac{\text{J} \cdot \text{J}}{\text{C}^2}\right)\left(\frac{\text{s}}{\text{J}}\right) = \left(\frac{\text{J}}{\text{C}}\right)\left(\frac{\text{s}}{\text{C}}\right) = \text{V} \frac{1}{\text{A}} = \Omega$

The units give ohms, which is the correct unit for resistance.

### 48. Frame the Problem

- The current flowing through the resistor will cause a power output.
- Power, potential difference, current, and resistance are all related.

### Identify the Goal

The power output

### Variables and Constants

Involved in the Problem	Known	Unknown
$R$	$I = 3.50 \text{ A}$	$P$
$P$	$R = 24.0 \Omega$	
$I$		

### Strategy

Use the relation between the power output, the resistance and the current flowing through the resistor.

Multiply.

An  $\text{A} \cdot \Omega$  is equivalent to a  $\text{W}$ , thus

The power output is  $294 \text{ W}$ .

### Calculations

$$P = I^2 R$$

$$P = (3.50 \text{ A})^2 (24.0 \Omega)$$

$$P = 294 \text{ W}$$

### Validate

Unit Check:  $\text{A}^2 \Omega = \text{A}(\text{A}\Omega) = \text{AV} = \text{W}$

The units give watts, which is the correct unit for power.

### 49. Frame the Problem

- The toaster will have a charge due to the potential difference applied.
- Electric Energy, potential difference, and charge are all related.
- Power, potential difference, and current are all related.

### Identify the Goal

The charge that passes through the toaster.

### Variables and Constants

Involved in the Problem	Known	Unknown
$V$	$P = 900 \text{ W}$	$V$
$P$	$I = 7.50 \text{ A}$	$Q$
$Q$	$\Delta E_Q = 2.40 \times 10^5 \text{ J}$	
$\Delta E_Q$		
$I$		

**Strategy**

Use the relation between the power output, the potential difference and the current to solve for the potential difference.

Divide.

$1 \frac{\text{W}}{\text{A}}$  is equivalent to 1 V, thus

Use the relation between the potential difference, the electric energy and the charge.

Solve for the charge.

Divide.

$1 \frac{\text{J}}{\text{V}}$  is equivalent to 1 C, thus

The charge that passed through the toaster is  $2.00 \times 10^3 \text{ C}$ .

**Calculations**

$$P = VI$$

$$\frac{P}{I} = \frac{V}{I} I$$

$$V = \frac{P}{I}$$

$$V = \frac{900 \text{ W}}{7.50 \text{ A}}$$

$$V = 120 \text{ V}$$

$$V = \frac{\Delta E_Q}{Q}$$

$$VQ = \frac{\Delta E_Q}{Q} Q$$

$$VQ = \Delta E_Q$$

$$\frac{VQ}{V} = \frac{\Delta E_Q}{V}$$

$$Q = \frac{\Delta E_Q}{V}$$

$$Q = \frac{2.40 \times 10^5 \text{ J}}{120 \text{ V}}$$

$$Q = 2000 \text{ C}$$

**Validate**

The units give coulombs, which is the correct unit for charge.

**50. Frame the Problem**

- The floodlight filament will have a power rating.
- Power, potential difference, and resistance are all related.
- There will be energy consumed by the floodlight filament.
- Electric energy, power, and time are all related.

**Identify the Goal**

**(a)** The power rating of the floodlight filament

**(b)** The energy consumed by the floodlight filament

**Variables and Constants****Involved in the Problem**

$R$

$P$

$V$

$\Delta t$

$\Delta E_Q$

**Known**

$R = 22.0 \Omega$

$V = 110 \text{ V}$

$\Delta t = 2.5 \text{ h}$

**Unknown**

$P$

$\Delta E_Q$

**Strategy**

Use the relation between the power output, the resistance and the potential difference.

Divide.

$1 \frac{\text{V}^2}{\Omega}$  is equivalent to 1 W, thus

**(a)** The power rating is 550 W.

**Calculations**

$$P = \frac{V^2}{R}$$

$$P = \frac{(110 \text{ V})^2}{22.0 \Omega}$$

$$P = 550 \text{ W}$$

**Strategy**

Convert the time into seconds.

Use the definition of power.

Solve for  $\Delta E_Q$ .

Multiply.

1 W·s is equivalent to 1 J, thus

Round up.

**(b)** The energy consumed is  $\Delta E_Q = 5.0 \times 10^6$  J.

**Calculations**

$$\Delta t = (60 \frac{\text{s}}{\text{min}}) \cdot (60 \frac{\text{min}}{\text{h}}) \cdot 2.5 \text{ h}$$

$$\Delta t = 9000 \text{ s}$$

$$P = \frac{\Delta E_Q}{\Delta t}$$

$$\Delta E_Q = P \Delta t$$

$$\Delta E_Q = (9000 \text{ s})(550 \text{ W})$$

$$\Delta E_Q = 4.95 \times 10^6 \text{ J}$$

$$\Delta E_Q = 5.0 \times 10^6 \text{ J}$$

**Validate**

The units give joules, which is the correct unit for energy.

**Solutions for Practice Problems****Student Textbook page 664****51. Frame the Problem**

- The total amount of electric energy the dryer uses in a specific amount of time depends on the power output.
- Power companies charge a specific amount of dollars per unit of energy used.

**Identify the Goal**

The cost, in cents, to dry a load of clothes

**Variables and Constants**

Involved in the Problem		Known	Unknown
$\Delta t$	Cost	$\Delta t = 25 \text{ min}$	Cost
$P$	$\Delta E_c$	Rate = 7.20 cents/kW·h	$\Delta E_c$
Rate		$P = 1280 \text{ W}$	

**Strategy**

Find the total time, in hours, that the dryer is on to dry a load of clothes.

Find the total amount of energy consumed by using the definition of power.

Find the cost.

Multiply.

The cost is 3.75 cents.

**Calculations**

$$t = (\frac{1}{60} \frac{\text{h}}{\text{min}}) \cdot 25.0 \text{ min}$$

$$t = 0.417 \text{ h}$$

$$P = \frac{\Delta E_c}{\Delta t}$$

Solve for  $\Delta E_c$  first

$$P \Delta t = \frac{\Delta E_c}{\Delta t} \Delta t$$

$$P \Delta t = \Delta E_c$$

$$\Delta E_c = (1250 \text{ W})(0.417 \text{ h})$$

$$\Delta E_c = 520 \text{ W} \cdot \text{h}$$

Substitute first

$$1250 \text{ W} = \frac{\Delta E_c}{0.417 \text{ h}}$$

$$(1250 \text{ W})(0.417 \text{ h}) = \frac{\Delta E_c}{0.417 \text{ h}} (0.417 \text{ h})$$

$$\Delta E_c = 520 \text{ W} \cdot \text{h}$$

$$\text{Cost} = \text{Rate} \cdot \Delta E_c$$

$$\text{Cost} = \frac{7.20 \text{ cents}}{\text{kW} \cdot \text{h}} 520 \text{ W} \cdot \text{h} \cdot \frac{1 \text{ kW}}{1000 \text{ W}}$$

$$\text{Cost} = 3.75 \text{ cents}$$

**Validate**

The units combine and cancel to give cents. As we can see by comparing with the model problem, the cost of using a dryer is much higher than watching television.

**52. Frame the Problem**

- The total amount of electric energy the blow dryer uses in a specific amount of time depends on the power output.
- The blow dryer's power output depends on its resistance and its current which are all related.
- Power companies charge a specific amount of dollars per unit of energy used.

**Identify the Goal**

The cost, in cents, to dry your hair

**Variables and Constants**

Involved in the Problem		Known	Unknown
$\Delta t$	Cost	$\Delta t = 12.0 \text{ min}$	Cost
$P$	$\Delta E_c$	Rate = 8.50 cents/kW·h	$\Delta E_c$
Rate	$R$	$R = 21.0 \Omega$	$P$
$I$		$I = 5.50 \text{ A}$	

**Strategy**

Use the relation between the power output, the resistance and the current flowing through the resistor.

Multiply.

An  $\text{A}^2 \cdot \Omega$  is equivalent to a W, thus

Find the total time, in hours, that the dryer is on to dry a load of clothes.

Find the total amount of energy consumed by using the definition of power.

Find the cost.

Multiply.

The cost is 1.08 cents.

**Validate**

The units combine and cancel to give cents. As we can see by comparing with the previous problem it cost less to dry your hair than to dry your clothes, which is reasonable.

**Calculations**

$$P = I^2 R$$

$$P = (5.50 \text{ A})^2 (21.0 \Omega)$$

$$P = 635 \text{ W}$$

$$t = \left(\frac{1}{60} \frac{\text{h}}{\text{min}}\right) \cdot 12.0 \text{ min}$$

$$t = 0.200 \text{ h}$$

$$P = \frac{\Delta E_c}{\Delta t}$$

Solve for  $\Delta E_c$  first

$$P \Delta t = \frac{\Delta E_c}{\Delta t} \Delta t$$

$$P \Delta t = \Delta E_c$$

$$\Delta E_c = (635 \text{ W})(0.200 \text{ h})$$

$$\Delta E_c = 127 \text{ W} \cdot \text{h}$$

Substitute first

$$635 \text{ W} = \frac{\Delta E_c}{0.200 \text{ h}}$$

$$(635 \text{ W})(0.200 \text{ h}) = \frac{\Delta E_c}{0.200 \text{ h}} (0.200 \text{ h})$$

$$\Delta E_c = 127 \text{ W} \cdot \text{h}$$

$$\text{Cost} = \text{Rate} \cdot \Delta E_c$$

$$\text{Cost} = \frac{8.50}{\text{kW} \cdot \text{h}} 127 \text{ W} \cdot \text{h} \frac{1 \text{ kW}}{1000 \text{ W}}$$

$$\text{Cost} = 1.08 \text{ cents}$$

**53. Frame the Problem**

- The electric kettle has a potential difference applied to it and a resistance, thus it has a power rating.
- The total amount of electric energy the electric kettle uses in a specific amount of time depends on the power output.
- Power companies charge a specific amount of dollars per unit of energy used.

**Identify the Goal**

- (a)** The power rating of the kettle
- (b)** The cost, in cents, to boil the water

**Variables and Constants**

Involved in the Problem	Known	Unknown
$R$	$R = 10.0 \Omega$	$P$
$P$	$V = 120 \text{ V}$	Cost
$V$	$\Delta t = 3.2 \text{ min}$	$\Delta E_c$
$\Delta t$	Rate = 6.5 cents/kW·h	
Cost		
$\Delta E_c$		
Rate		

**Strategy**

Use the relation between the power output, the resistance and the potential difference.

Divide.

$1 \frac{\text{V}^2}{\Omega}$  is equivalent to 1 W, thus

- (a)** The power rating is  $1.4 \times 10^3 \text{ W}$ .

The answer here is correct. The textbook will be changed at next printing to reflect correct answer.

**Strategy**

Find the total time, in hours, that the kettle is on.

Find the total amount of energy consumed by using the definition of power.

**Calculations**

$$P = \frac{V^2}{R}$$

$$P = \frac{(120 \text{ V})^2}{10.0 \Omega}$$

$$P = 1.4 \times 10^3 \text{ W}$$

**Calculations**

$$t = \left(\frac{1}{60} \frac{\text{h}}{\text{min}}\right) \cdot 3.2 \text{ min}$$

$$t = 0.053 \text{ h}$$

$$P = \frac{\Delta E_c}{\Delta t}$$

Solve for  $\Delta E_c$  first

$$P \Delta t = \frac{\Delta E_c}{\Delta t} \Delta t$$

$$P \Delta t = \Delta E_c$$

$$\Delta E_c = (1.4 \times 10^3 \text{ W})(0.053 \text{ h})$$

$$\Delta E_c = 76.8 \text{ W}\cdot\text{h}$$

Substitute first

$$1.4 \times 10^3 \text{ W} = \frac{\Delta E_c}{0.053 \text{ h}}$$

$$(1.4 \times 10^3 \text{ W})(0.053 \text{ h})$$

$$= \frac{\Delta E_c}{0.053 \text{ h}}(0.053 \text{ h})$$

$$\Delta E_c = 76.8 \text{ W}\cdot\text{h}$$

Find the cost.

$$\text{Cost} = \text{Rate} \cdot \Delta E_c$$

Multiply and round up.

$$\text{Cost} = \frac{6.5 \text{ cents}}{\text{kW}\cdot\text{h}} 76.8 \text{ W}\cdot\text{h} \frac{1 \text{ kW}}{1000 \text{ W}}$$

$$\text{Cost} = 0.50 \text{ cents}$$

(b) The cost is 0.50 cents.

### Validate

The units combine and cancel to give cents.

## Problems for Understanding

Student Textbook page 667

24. If the voltage increases from 32.0 V to 120 V, there will be 3.75 times more current.

$$\text{The initial current} = \frac{\text{power}}{\text{voltage}} = \frac{200 \text{ W}}{32.0 \text{ V}} = 6.25 \text{ A}$$

$$\text{The new current} = 3.75 \times 6.25 \text{ A} = 23.4 \text{ A}$$

$$\text{The new power} = VI = 120 \text{ V} \times 23.4 \text{ A} = 2810 \text{ W}$$

25. (a)  $I = \frac{P}{V}$

$$I = \frac{1400 \text{ W}}{120 \text{ V}}$$

$$I = 12 \text{ A}$$

(b)  $Q = IT$

$$Q = 11.7 \text{ A} \times (60 \times 3.60) \text{ s}$$

$$Q = 2.5 \times 10^3 \text{ C}$$

(c)  $E = PT$

$$E = 1400 \text{ W} \times (60 \times 3.60) \text{ s}$$

$$E = 3.0 \times 10^5 \text{ J}$$

26.  $E = P\Delta t$

$$P = IV$$

$$E = IV\Delta t$$

$$E = 6.25 \text{ A} \times 240 \text{ V} \times (60 \times 5.50) \text{ s}$$

$$E = 5.0 \times 10^5 \text{ J}$$

27.  $E = PT$

$$E = \frac{V^2}{R} \times T$$

$$E = \frac{(125 \text{ V})^2}{15.0 \Omega} \times \left(\frac{12.0}{60}\right) \text{ h}$$

$$E = 208 \text{ W}\cdot\text{h}$$

$$\text{Cost} = E \times \$0.0850/\text{kW}\cdot\text{h}$$

$$\text{Cost} = 0.208/\text{kW}\cdot\text{h} \times \$0.0850/\text{kW}\cdot\text{h}$$

$$\text{Cost} = \$0.0177 = 1.77 \text{ cents}$$

28.

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{25 \Omega} = \frac{1}{75 \Omega} + \frac{1}{R_2}$$

$$\frac{1}{25 \Omega} - \frac{1}{75 \Omega} = \frac{1}{R_2}$$

$$R_2 = 37.5 \Omega$$

$$\begin{aligned}
 29. \quad \frac{1}{R_{2+3}} &= \frac{1}{R_2} + \frac{1}{R_3} \\
 \frac{1}{R_{2+3}} &= \frac{1}{30.0 \, \Omega} + \frac{1}{6.00 \, \Omega} \\
 \frac{1}{R_{2+3}} &= \frac{6}{30.0 \, \Omega} \\
 \frac{1}{R_{2+3}} &= 5.00 \, \Omega \\
 R_{eq} &= R_{2+3} + R_1 \\
 R_{eq} &= 5.00 \, \Omega + 25.0 \, \Omega \\
 R_{eq} &= 30.0 \, \Omega \\
 I_T = I_1 = \frac{V_T}{R_{eq}} &= \frac{180 \, \text{V}}{30.0 \, \Omega} = 6.0 \, \text{A} \\
 V_1 = I_1 R_1 &= 6.0 \, \text{A} \times 25.0 \, \Omega = 150 \, \text{V} \\
 V_{2+3} = V_T - V_1 &= 180 \, \text{V} - 150 \, \text{V} = 30.0 \, \text{V} \\
 V_2 &= 30.0 \, \text{V} \\
 V_3 &= 30.0 \, \text{V} \\
 I_2 = \frac{V_2}{R_2} &= \frac{30.0 \, \text{V}}{30.0 \, \Omega} = 1.0 \, \text{A} \\
 I_3 = \frac{V_3}{R_3} &= \frac{30.0 \, \text{V}}{6.00 \, \Omega} = 5.0 \, \text{A}
 \end{aligned}$$

30. Power in = Power out

$$\begin{aligned}
 VI &= \frac{mgh}{T} \\
 T &= \frac{mgh}{VI} \\
 T &= \frac{5.00 \, \text{kg} \times 9.8 \, \text{m/s}^2 \times 35.0 \, \text{m}}{36.0 \, \text{V} \times 4.80 \, \text{A}} \\
 T &= 9.9 \, \text{s}
 \end{aligned}$$

$$\begin{aligned}
 31. \quad \text{(a)} \quad R &= \rho \frac{L}{A} = (1.7 \times 10^{-8} \, \Omega \cdot \text{m}) \frac{2 \times 45.0 \, \text{m}}{3.14 \times (.00051 \, \text{m})^2} \\
 R &= 1.9 \, \Omega \\
 \text{(b)} \quad P &= \frac{V^2}{R} \\
 R &= \frac{V^2}{P} = \frac{(120 \, \text{V})^2}{100 \, \text{W}} = 144 \, \Omega = 1.4 \times 10^2 \, \Omega \\
 \text{(c)} \quad I &= \frac{V_T}{R_T} = \frac{120 \, \text{V}}{(144 + 1.9) \, \Omega} = 0.8225 \, \text{A} = 0.82 \, \text{A} \\
 \text{(d)} \quad P &= VI = 120 \, \text{V} \times 0.82 \, \text{A} = 98 \, \text{W}
 \end{aligned}$$

32. The *emf* of the battery remains constant, regardless of the resistance in the circuit.

Therefore:

$$\begin{aligned}
 V_s + V_{\text{int}} &= E \\
 24.0 \, \text{V} + (I_s \times r) &= E \\
 24.0 \, \text{V} + \left(\frac{V_s}{R_s} \times r\right) &= E \\
 24.0 \, \text{V} + \left(\frac{24.0 \, \text{V}}{40.0 \, \Omega}\right) r &= E \\
 24.0 \, \text{V} + 0.60r &= E
 \end{aligned}$$

Similarly for the second resistance of  $15.0 \, \Omega$ , we get:

$$V_s + V_{\text{int}} = E$$

$$23.5 \text{ V} + (I_s \times r) = E$$

$$23.5 \text{ V} + \left(\frac{V}{R} \times r\right) = E$$

$$23.5 \text{ V} + \left(\frac{23.5 \text{ V}}{15.0 \Omega}\right) r = E$$

$$23.5 \text{ V} + 1.57r = E$$

Solving for  $r$  in these simultaneous equations, we get

$$23.5 \text{ V} + 1.57r = 24.0 \text{ V} + 0.60r$$

$$0.97r = 0.50$$

$$r = 0.52 \Omega$$

The internal resistance of the battery is  $0.52 \Omega$ .

The *emf* of the battery can be found by substitution of  $r$  in either equation:

$$E = 23.5 \text{ V} + 1.57r$$

$$E = 23.5 \text{ V} + (1.57 \times 0.52 \Omega)$$

$$E = 24.3 \text{ V}$$